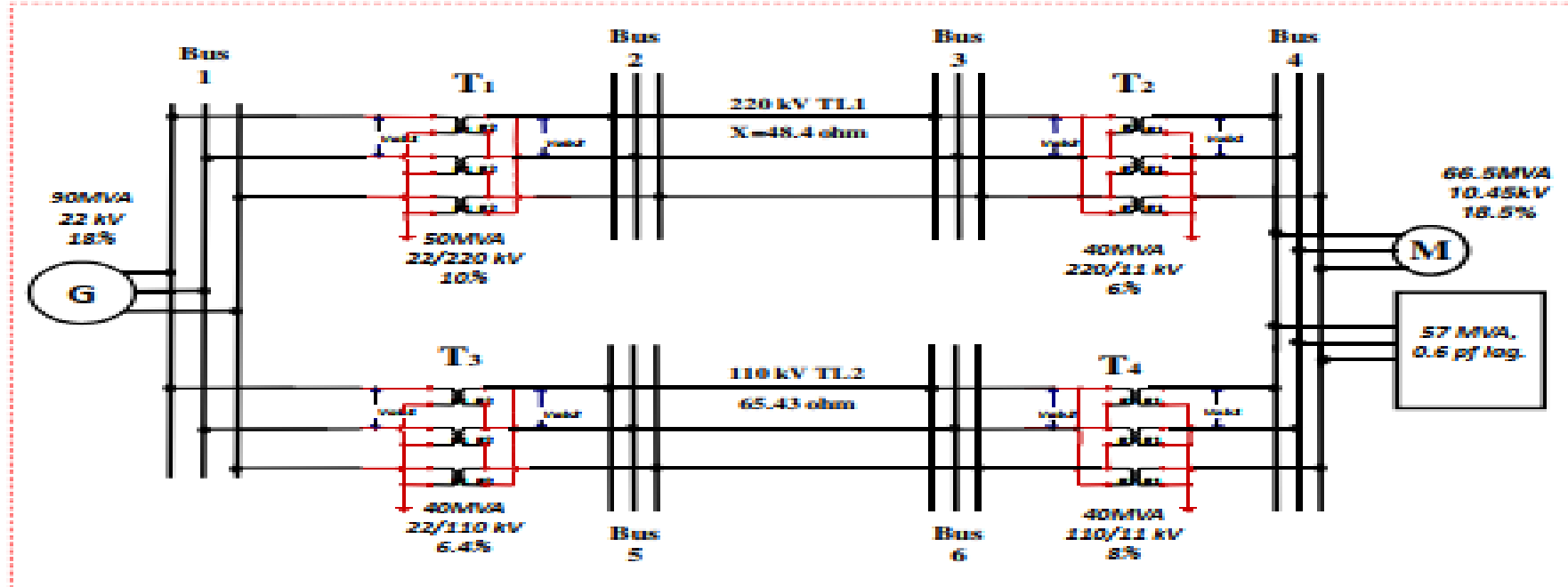


Lec_02



PER UNIT SYSTEM

PROBLEM:

Draw the single-line diagram of a three phase power system.



Solution:

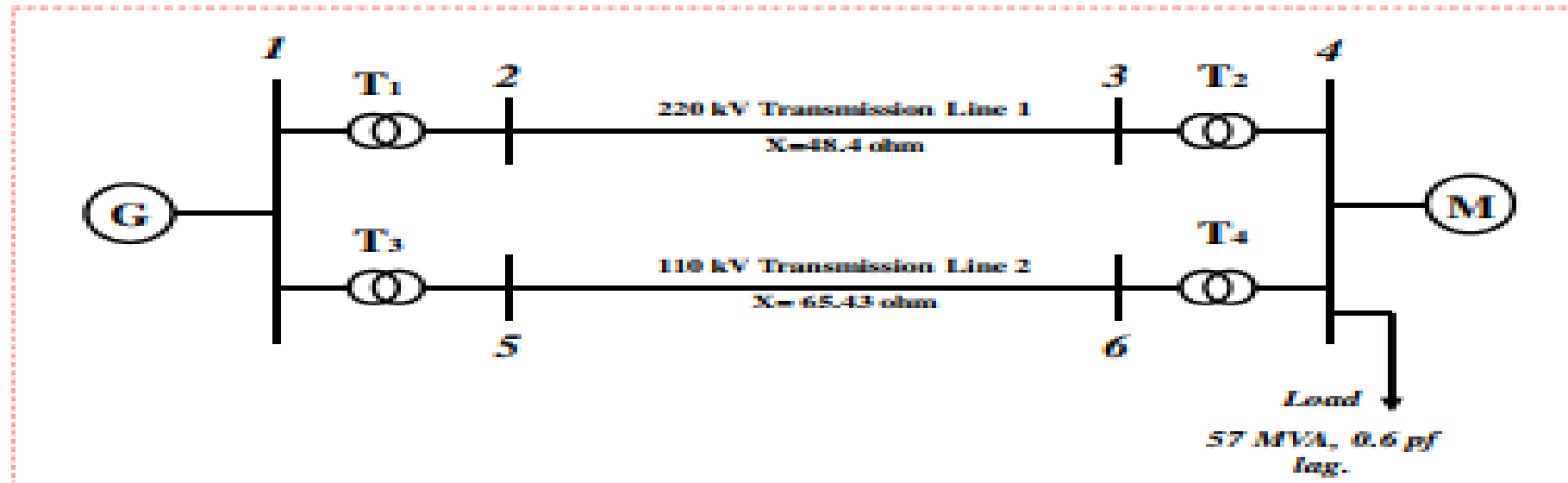
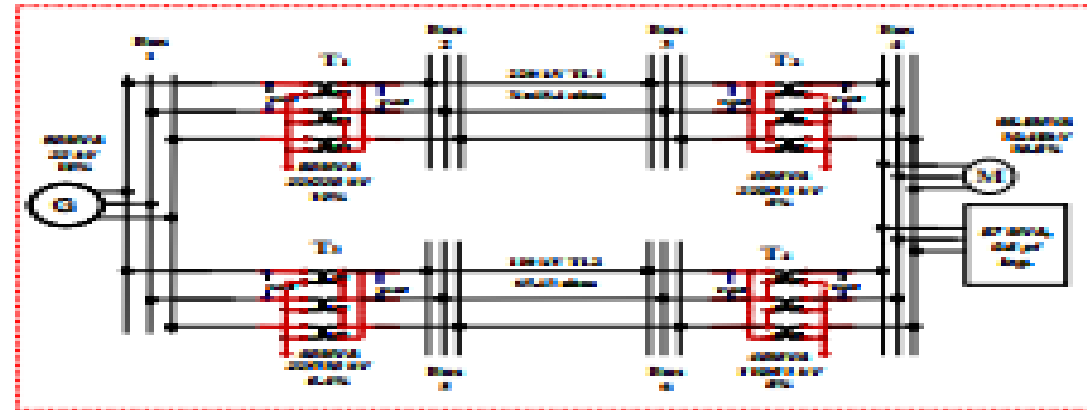


THE PER UNIT SYSTEM

Analyzing interconnected three-phase power systems having *different voltage levels* require huge transformation of all impedances to a single voltage level.


NOTE:

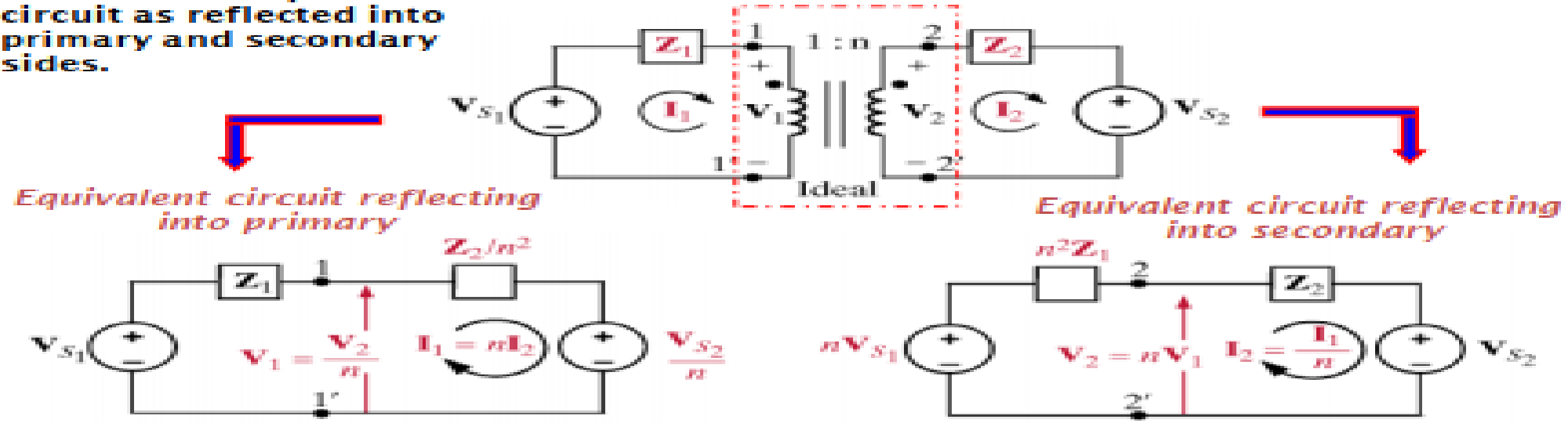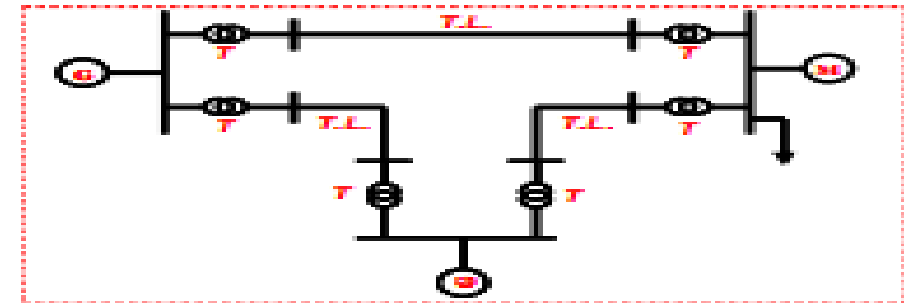Transformer equivalent circuit as reflected into primary and secondary sides.



This **large mathematical work** can be avoided by utilizing the **per unit system**. Various physical quantities such as power, voltage, current and impedance are expressed as a decimal fraction of base quantities.

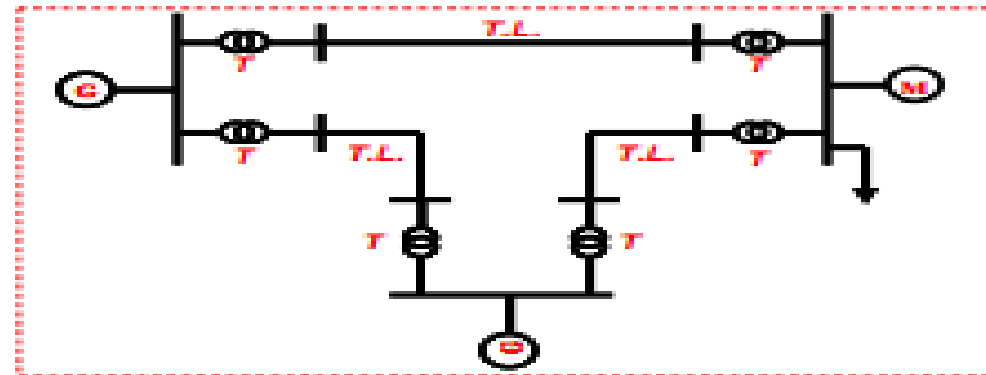The numerical per unit value of any quantity is its ratio to a chosen base quantity of the same dimension. Thus a per unit quantity is a **normalized** quantity with respect to the chosen base value. The per unit value of a quantity is thus defined as:



$$p.u. \text{ value} = \frac{\text{Actual Value}}{\text{Base Value}}$$

Note:

The **nominal voltage** of lines and equipment is almost always known as well as the **apparent (complex) power** in megavolt-amperes, so these two quantities are usually chosen for base value calculation. A minimum of four base quantities are required to complete the per unit system: volt-ampere, voltage, current and impedance. **Usually three phase MVA and line-to-line voltages are selected for as:**

$(S_{Base})_{3\phi}$ The **base complex power** in mega-volt-amperes (MVA)

$(V_{Base})_{LL}$ the **base voltage** in kilovolts

$$|S_{Base}|_{3\phi} = \sqrt{3} |I_{base}| |V_{Base}|_{LL} \quad \text{MVA}$$

The **base current** in kiloamperes

$$|I_{base}|_L = \frac{|S_{Base}|_{3\phi}}{\sqrt{3} |V_{Base}|_{LL}}$$

NOTE

$$(S_{Base})_{1\phi} = \frac{(S_{Base})_{3\phi}}{3}$$

$$|S_{Base}|_{1\phi} = |I_{base}|_{\phi} |V_{Base}|_{\phi}$$

$$|V_{Base}|_{1\phi} = \frac{|V_{Base}|_{3\phi}}{\sqrt{3}}$$

The *base impedance* will also be given by

$$|Z_{Base}| = \frac{|V_{Base}|_{\phi}}{|I_{base}|_{\phi}} = \frac{|V_{Base}|_{\phi}^2}{|S_{base}|_{\phi}} \text{ ohms}$$

$$|Z_{base}| = \frac{\left[\frac{|V_{Base}|_{LL}}{\sqrt{3}} \right]^2}{\left[\frac{|S_{Base}|_{3\phi}}{3} \right]} = \frac{[|V_{Base}|_{LL}]^2}{[|S_{Base}|_{3\phi}]}$$

From the definition of per unit values: $p.u. \text{ value} = \frac{\text{Actual Value}}{\text{Base Value}}$

$$S_{p.u.} = \frac{S}{S_{Base}}$$

$$V_{p.u.} = \frac{V}{V_{Base}}$$

$$I_{p.u.} = \frac{I}{I_{Base}}$$

The per unit impedance:

$$Z_{p.u.} = \frac{Z_{\Omega}}{Z_{Base}} = \frac{Z_{\Omega} |S_{Base}|}{|V_{Base}|^2} p.u.$$

NOTE

The impedance could
be presented in
pu or %
0.2 pu \leftrightarrow 20%

Base Conversions

If $(Z_{p.u.})_{old}$ an impedance in per unit on a given **old base**

and $(I_{Base})_{old}$ the base current in kiloamperes

$(V_{Base})_{old}$ the base voltage in kilovolts


It is sometimes required to obtain the per unit value referred to a **new base** set.

The conversion expression is obtained as:

$$(Z_{p.u.})_{new} = (Z_{p.u.})_{old} \frac{|(S_{Base})_{new}|}{|(S_{Base})_{old}|} \cdot \frac{|(V_{Base})_{old}|^2}{|(V_{Base})_{new}|^2} \text{ p.u.}$$

If the **volt bases are the same**, then

$$(Z_{p.u.})_{new} = (Z_{p.u.})_{old} \frac{|(S_{Base})_{new}|}{|(S_{Base})_{old}|} \text{ p.u.}$$

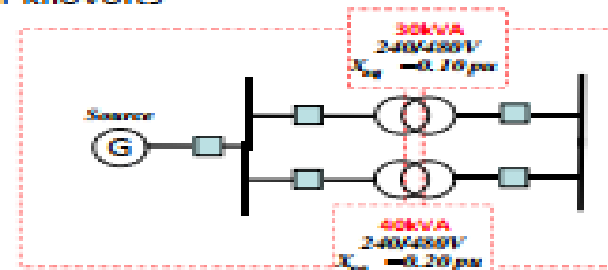

Per unit System :-

$$\left| \frac{S}{V} \right| \quad \left| \frac{I}{Z} \right|$$

↓
Two value
taken.

↓
Extracted.

$$\left. \begin{array}{l} S_{base} \\ V_{base} \end{array} \right\} \Rightarrow$$

$$\boxed{I_{base} = \frac{S_{base}}{\sqrt{3} V_{base LL}}}$$

$$\boxed{|Z_{base}| = \frac{V_{base \phi}}{I_{base \phi}} = \frac{|V_{base}|^2}{|S_{base}|_{\phi}}}$$

$$S = VI$$
$$I = \frac{S}{V}$$

$$\boxed{|Z_{base}| = \frac{\left[\frac{V_{base}}{\sqrt{3}} \right]^2}{\frac{S_{base}}{3}} = \frac{\left[V_{base LL} \right]^2}{S_{base 3\phi}}}$$

Per unit Value = $\frac{\text{Actual Value}}{\text{Base Value}}$

$V = .9 \text{ p.u.}$

$I = .8 \text{ p.u.}$

$S_{\text{p.u.}} = \frac{S}{S_{\text{Base}}}$ ✓

$V_{\text{p.u.}} = \frac{V}{V_{\text{Base}}}$ ✓

$I_{\text{p.u.}} = \frac{I}{I_{\text{Base}}}$ ✓

$Z_{\text{p.u.}} = \frac{Z}{Z_{\text{Base}}}$ ✓

$$Z_{pu} = \frac{Z_{\Omega}}{Z_{Base}}$$

$$Z_{Base} = \frac{V_{Base}^2}{S_{Base}}$$

$$Z_{pu} = \frac{Z_{\Omega}}{\frac{V_{Base}^2}{S_{Base}}}$$

$$Z_{pu} = \frac{Z_{\Omega} \cdot |S_{Base}|}{|V_{Base}|^2} \text{ P.U.}$$

Base Conversion:-

⇒ [Convert The P.U. in new Base Value.

$$Z_{PU_{new}} = \frac{Z_{\cancel{S} \cancel{V}}_{old}}{Z_{Base_{new}}}$$

$$= \frac{(Z_{PU})_{old} \cdot |V_{Base_{old}}|^2}{|S_{Base_{old}}|}$$

$$= \frac{(Z_{PU_{old}}) \cdot |V_{Base_{old}}|^2}{|S_{Base_{old}}|} \cdot \frac{|S_{Base_{new}}|}{|V_{Base_{new}}|^2}$$

$$Z_{PU_{new}} = Z_{PU_{old}} \cdot \frac{|V_{Base_{old}}|^2}{|V_{Base_{new}}|^2} \cdot \frac{|S_{Base_{new}}|}{|S_{Base_{old}}|}$$

$$Z_{PU_{old}} = \frac{Z_{\cancel{S} \cancel{V}}_{old} \cdot S_{Base}}{|V_{Base}|^2}$$

$$Z_{PU_{old}} \cdot \frac{|V_{Base_{old}}|^2}{S_{Base_{old}}} = Z_{\cancel{S} \cancel{V}}$$

if voltage are
Same .

$$(Z_{pu})_{new} = (Z_{pu})_{old} \cdot \frac{|S_{base}|_{new} \text{ pu.}}{|S_{base}|_{old}}$$

Example # 01 :

$$Z = 3.346 + j77.299 \Omega.$$

$$\text{Base} \begin{cases} S = 100 \text{ MVA} \\ V = 735 \text{ kV} \end{cases}$$


$$Z_{pu} = Z \Omega \cdot \frac{S_{\text{Base}}}{|V_{\text{Base}}|^2} \text{ P.U.}$$

$$= Z \Omega \cdot \frac{100 \times 10^6}{(735 \times 10^3)^2}$$

$$= (3.346 + j77.299) \cdot \frac{100 \times 10^6}{(735 \times 10^3)^2}$$

$$= 6.19372 \times 10^{-4} + j1.43 \times 10^{-2}$$

Example #03

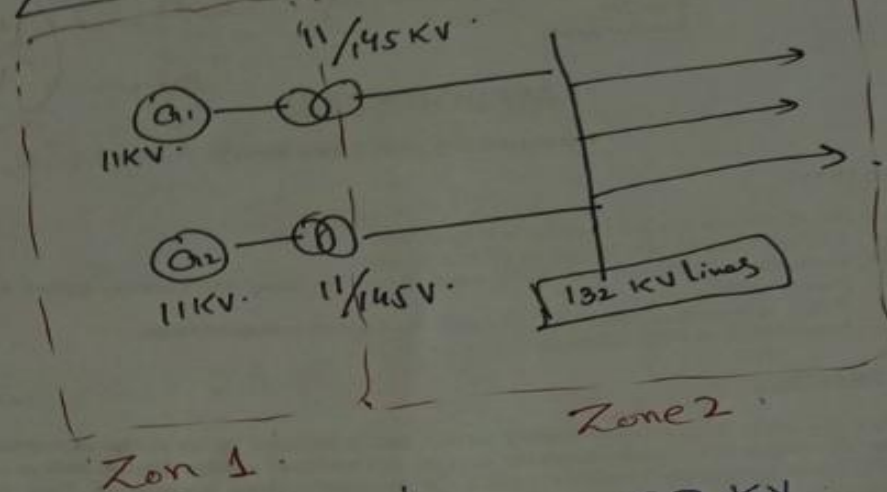

$$V_{base} = \frac{11}{145} (132)$$

132 KV
V_{base}

S_{Base} = 100 MVA → Same → All over current
V_{Base} = 132 KV

⇒ Different when move different Zones.

(ii) Now Convert
Reactances into new values.

Generator Reactance:-

$$Z_{pu\ old} = .26 \text{ p.u.}$$

$$\begin{aligned} Z_{new} &= .26 \times \frac{S_{new}}{S_{old}} \times \frac{|V_{old}|^2}{|V_{new}|^2} \\ &= .26 \times \frac{150}{66.6} \times \frac{(11)^2}{(10.01)^2} = .47 \text{ p.u.} \end{aligned}$$

Transformer Reactance:-

$$\begin{aligned} Z_{new} &= .125 \times \frac{150}{75} \times \frac{(145)^2}{(132)^2} \\ &= .201 \text{ p.u.} \end{aligned}$$

Example 1:

Consider a transmission line with an impedance $Z = 3.346 + j77.299$ ohm. Assume that Base MVA is 100 and Base kV is 735. What is the pu impedance.

Solution:

$$Z_{p.u.} = \frac{Z_{\Omega}}{Z_{Base}} = \frac{Z_{\Omega} |S_{Base}|}{|V_{Base}|^2} p.u.$$

$$Z_{p.u.} = \frac{Z_{\Omega} |MVA, S_{Base}|}{|kV, V_{Base}|^2} p.u. = \frac{Z_{\Omega} |100|}{|735|^2} = (Z_{\Omega}) * (1.85108 \times 10^{-4})$$

For $R = 3.346$ ohms we obtain

$$R_{p.u.} = (3.346)(1.85108 \times 10^{-4}) = 6.19372 \times 10^{-4}$$

For $X = 77.299$ ohms, we obtain

$$X_{p.u.} = (77.299)(1.85108 \times 10^{-4}) = 1.430867 \times 10^{-2}$$

Example 2: Convert the impedance of the previous example using a **new base** of 200 MVA and 345 kV.


$$(Z_{p.u.})_{old} = 6.19372 \times 10^{-4} + j1.430867 \times 10^{-2}$$

The **old base** is: 100 MVA and 735 kV. & The **new base** is: 200 MVA and 345 kV.

$$(Z_{p.u.})_{new} = (Z_{p.u.})_{old} \frac{|(S_{Base})_{new}|}{|(S_{Base})_{old}|} \cdot \frac{|(V_{Base})_{old}|^2}{|(V_{Base})_{new}|^2} p.u.$$

$$(Z_{pu})_{new} = (Z_{p.u.})_{old} \left[\frac{200}{100} \right] \left[\frac{735}{345} \right]^2 p.u.$$
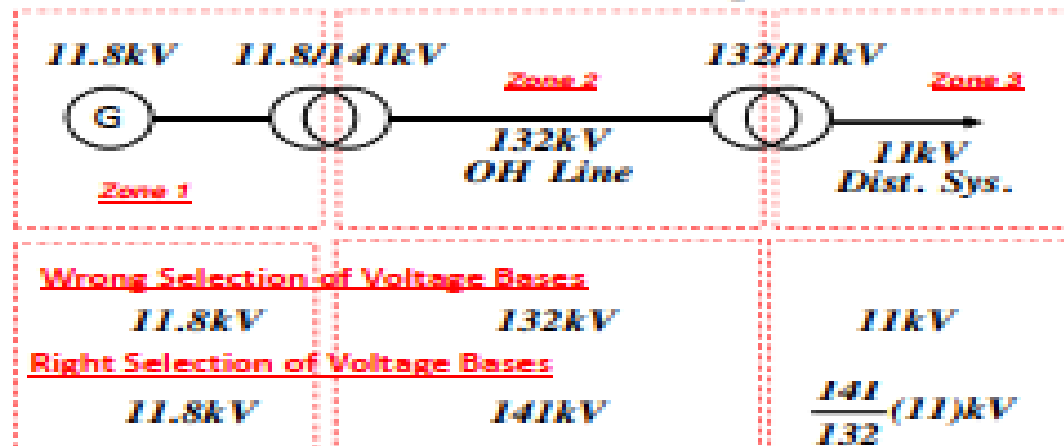
$$(Z_{pu})_{new} = 9.0775 (Z_{pu})_{old}$$




NOTE: kV Base Selection

The base voltages in the three circuits (**zones**) are related by the turns ratios of the intervening transformers. The transformers quoted may be different from the turns ratios for example a 220/33 kV (nominal) transformer may have a turns ratio of 220/34.5 kV.

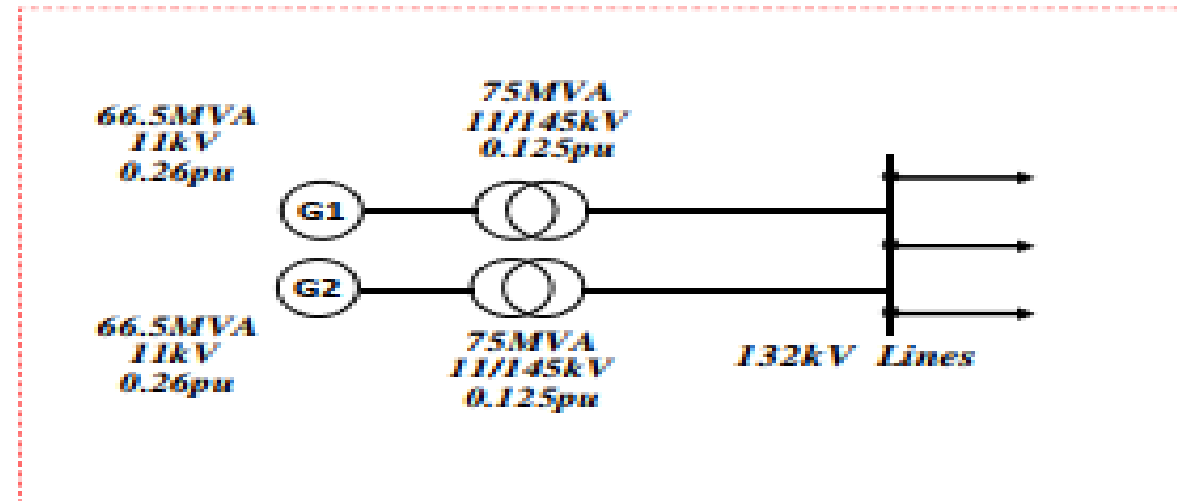Example 3:

Generators G1 and G2 have a *sub-transient reactance* of 26% on 66.6MVA rating at 11kV, and transformers T1 and T2 a voltage ratio of 11/145kV and an impedance of 12.5% on 75MVA. Choosing 100MVA as base MVA and 132kV as base voltage, find the percentage impedances to new base quantities.



Example 3: Generators G1 and G2 have a *sub-transient reactance* of 26% on 66.6MVA rating at 11kV, and transformers T1 and T2 a voltage ratio of 11/145kV and an impedance of 12.5% on 75MVA. Choosing 100MVA as base MVA and 132kV as base voltage, find the percentage impedances to new base quantities.

Solution: $S_{Base} = 100 \text{ MVA}$

$V_{Base}^{Zone 2} = 132 \text{ kV}$ At overhead Lines

$$\frac{[V_{Base}]_{Gen}^{Zone 1}}{[V_{Base}]_{OHL}^{Zone 2}} = \frac{[V_{T1}]_{Primary}}{[V_{T1}]_{Secondary}} = \frac{11}{145}$$

$$[V_{Base}]_{Gen}^{Zone 1} = \frac{11}{145} (132) = 10.01 \text{ kV}$$


$$(Z_{p.u.})_{new} = (Z_{p.u.})_{old} \cdot \frac{1(S_{Base})_{new}}{1(S_{Base})_{old}} \cdot \frac{1(V_{Base})_{old}^2}{1(V_{Base})_{new}^2} \text{ p.u.}$$

a. Generator reactance to new bases is:

$$(Z)_{new} = 26 \cdot \frac{100}{66.6} \cdot \frac{(11)^2}{(10.01)^2} = 47.24\% = 0.4724 \text{ pu}$$

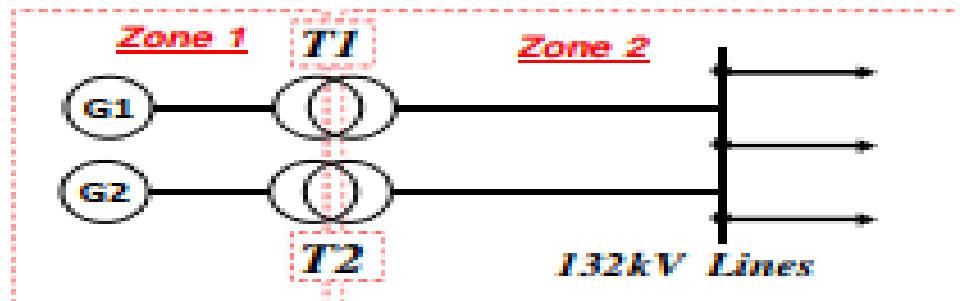b. Transformer reactance to new bases is:

$$(Z)_{new} = 12.5 \cdot \frac{100}{75} \cdot \frac{(145)^2}{(132)^2} = 20.1\% = 0.201 \text{ pu}$$




$T_1 \text{ \& } T_2$
rating
75MVA
11/145kV

NOTE

$Z = 26\%$
Is equivalent to
 $Z = 0.26 \text{ pu}$

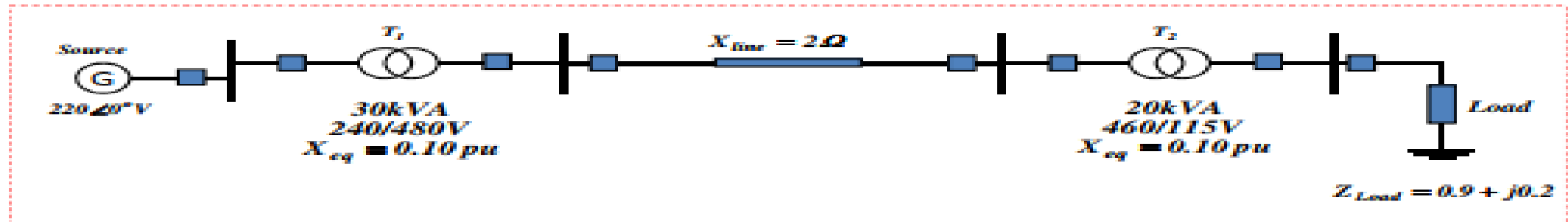Example 4:

For the system shown in the figure. Selecting the base values of **30KVA** and **240 V** at the generator side.



1. Find all the bases for the system.

S_{Base} , V_{Base} , I_{Base} and Z_{Base}

2. Draw the per unit reactance circuit.


3. Find the **actual value** of the load current

Reminder

How many zones do we have in this system?

Do you think the selected base voltages in the system zones are related by to the transformers and generator voltages.

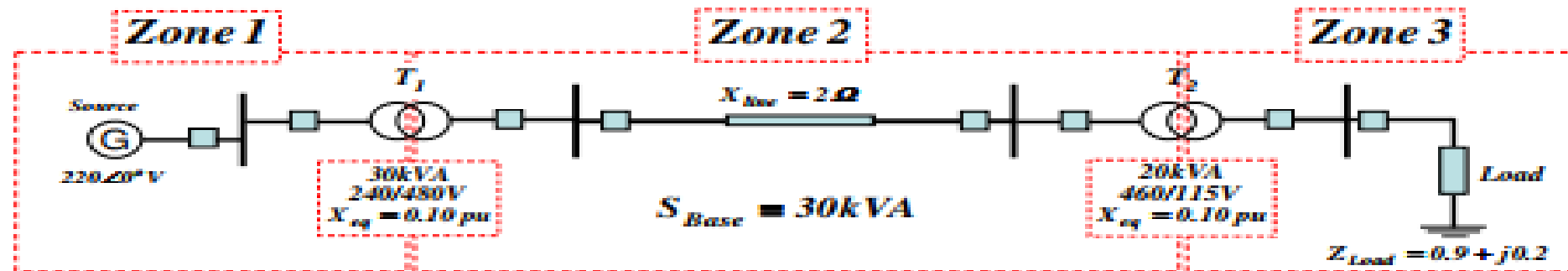Do we have impedances in pu, % or in ohms?



The bases for the system:

$$S_{Base} = 30 \text{ kVA}$$

$$[V_{Base}]_1 = 240 \text{ V}$$

$$\frac{[V_{Base}]_2}{[V_{Base}]_1} = \frac{480 \text{ V}}{240 \text{ V}}$$

$$[V_{Base}]_2 = [V_{Base}]_1 \frac{480 \text{ V}}{240 \text{ V}} = 480 \text{ V}$$

$$\frac{[V_{Base}]_3}{[V_{Base}]_2} = \frac{115 \text{ V}}{460 \text{ V}}$$

$$[V_{Base}]_3 = [V_{Base}]_2 \frac{115 \text{ V}}{460 \text{ V}} = 120 \text{ V}$$

$$[Z_{Base}]_1 = \frac{[V_{Base}]_1^2}{[S_{Base}]_1} = \frac{240^2}{30000} = 1.92 \Omega$$


$$[I_{Base}]_1 = \frac{[S_{Base}]_1}{\sqrt{3}[V_{Base}]_1} = \frac{30000}{\sqrt{3} 240} = 72.2 \text{ A}$$

$$[Z_{Base}]_2 = \frac{[V_{Base}]_2^2}{[S_{Base}]_2} = \frac{480^2}{30000} = 7.68 \Omega$$

$$[I_{Base}]_2 = \frac{[S_{Base}]_2}{\sqrt{3}[V_{Base}]_2} = \frac{30000}{\sqrt{3} 480} = 36.2 \text{ A}$$

$$[Z_{Base}]_3 = \frac{[V_{Base}]_3^2}{[S_{Base}]_3} = \frac{120^2}{30000} = 0.48 \Omega$$
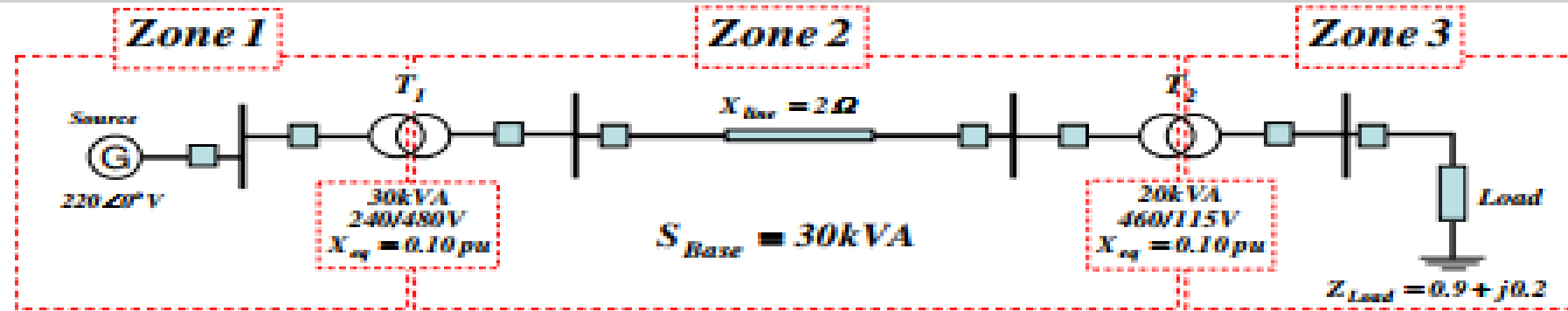
$$[I_{Base}]_3 = \frac{[S_{Base}]_3}{\sqrt{3}[V_{Base}]_3} = \frac{30000}{\sqrt{3} 120} = 144.3 \text{ A}$$



Draw the per unit circuit


Zone 1

$$S_{Base} = 30kVA$$

$$[V_{Base}]_1 = 240V$$

$$|Z_{Base}| = \frac{|V_{Base}|^2}{|S_{base}|} \text{ ohms}$$

$$[Z_{Base}]_1 = 1.92\Omega$$

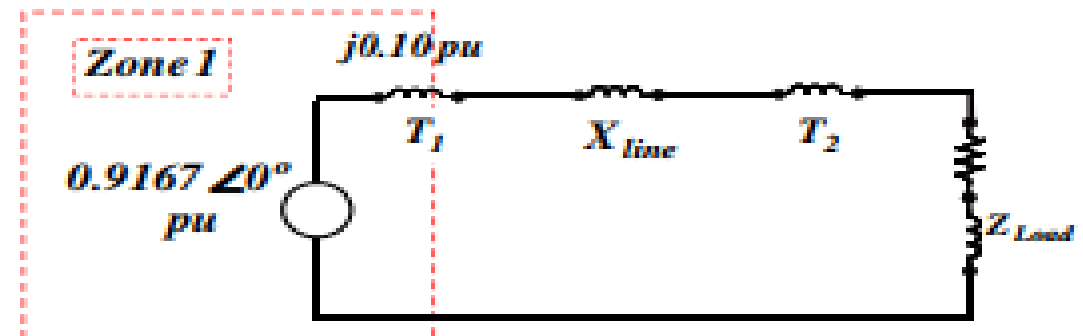

$$X_{T1} = j0.10 \text{ pu}$$

T1 Rating

30kVA


240/480V

Selected Bases

$S_{Base} = 30kVA$

$V_{Base1} = 240V$
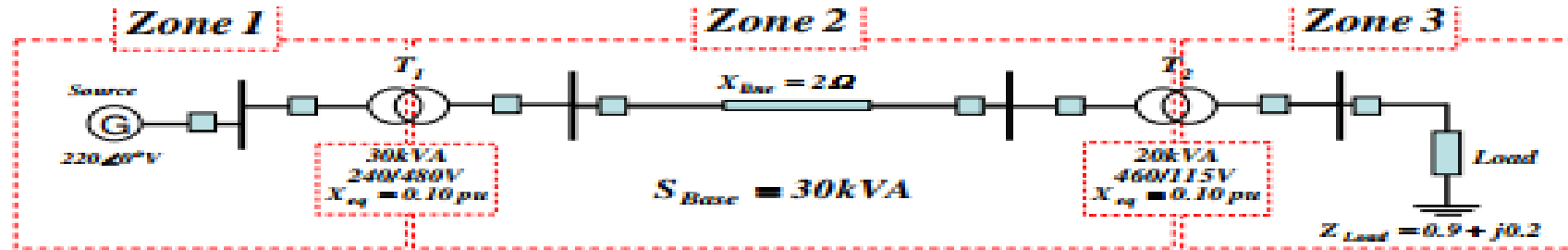
$$[V_{Source}]_{pu} = \frac{[V_{source}]_{actual}}{[V_{Base}]_1} = \frac{220\angle 0}{240} = 0.9167\angle 0^\circ \text{ pu}$$



Draw the per unit circuit


Zone 2

$$S_{Base} = 30 \text{ kVA}$$

$$[V_{Base}]_2 = 480 \text{ V}$$

$$|Z_{Base}| = \frac{|V_{Base}|^2}{|S_{Base}|} \text{ ohms}$$


$$[Z_{Base}]_2 = 7.68 \Omega$$

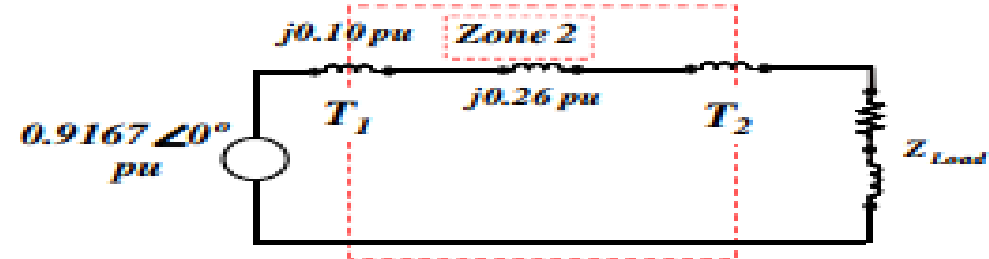

$$X_{line} = 2 \Omega$$

$$[X_{line}]_{pu} = \frac{2 \Omega}{[Z_{Base}]_2} = \frac{2}{7.68}$$

$$[X_{line}]_{pu} = 0.26 \text{ pu}$$

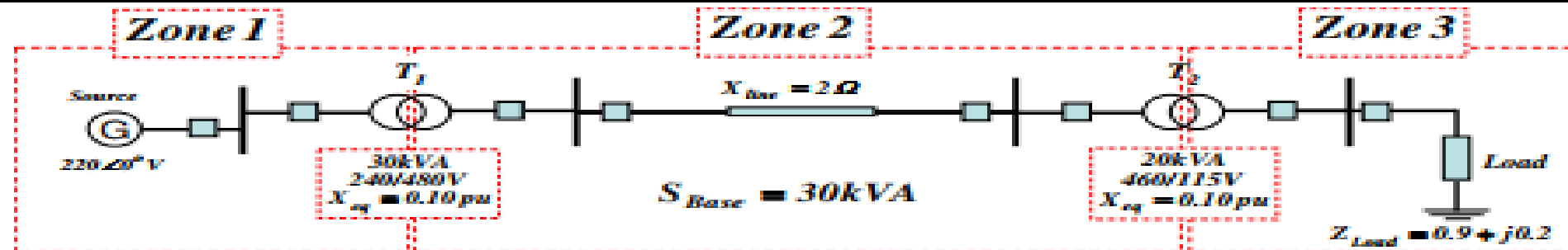

Draw the per unit circuit

Zone 3

$S_{Base} = 30 \text{ kVA}$

$$\frac{[V_{Base}]_2}{[V_{Base}]_3} = \frac{460}{115}$$

$$[V_{Base}]_2 = 480 \text{ V}$$

$$\frac{480}{[V_{Base}]_3} = \frac{460}{115}$$

$$[V_{Base}]_3 = 120 \text{ V}$$

$$[X_{T_2}]_{pu} = [X_{Old}]_{pu} \frac{[S_{Base}]_{New}}{[S_{Base}]_{Old}} \frac{[V_{Base}]_{Old}^2}{[V_{Base}]_{New}^2}$$

$$[X_{T_2}]_{pu} = 0.10 \frac{(30000) 115^2}{(20000) 120^2} = 0.1378 \text{ pu}$$

$$|Z_{Base}| = \frac{|V_{Base}|^2}{|S_{base}|} \text{ ohms}$$


$$[Z_{Base}]_3 = 0.48 \Omega$$

$$[Z_{load}]_{pu} = \frac{0.9 + j0.2}{0.48}$$



$$[Z_{load}]_{pu} = 1.875 + j0.4167 \text{ pu}$$

T2	Rating
	20kVA
	460/115V

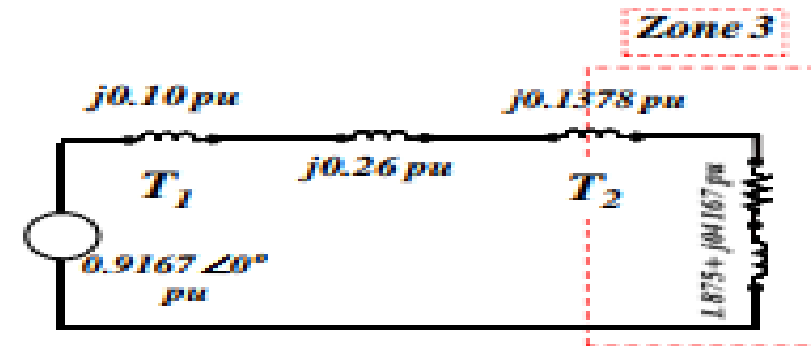Selected Bases
$S_{Base} = 30 \text{ kVA}$
$V_{Base3} = 120 \text{ V}$



2. The per unit reactance circuit.

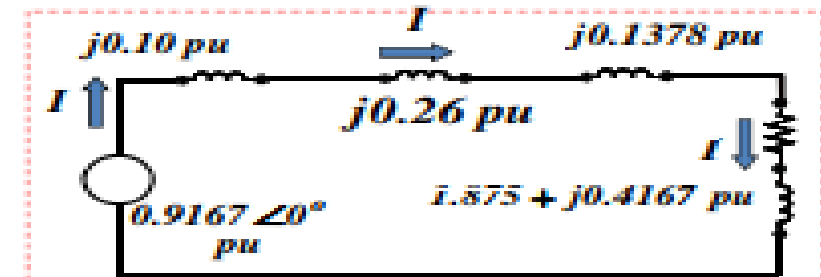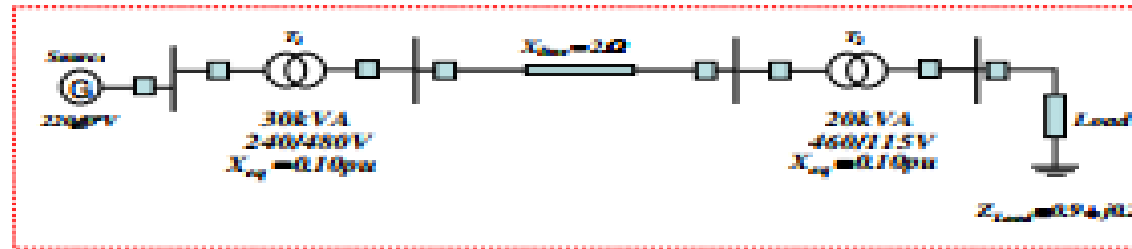

3. The actual load current

$$I_{pu} = \frac{V_{pu}}{(Z_{Total})} = \frac{0.9167 \angle 0^\circ}{j0.1 + j0.26 + j0.1378 + 1.875 + j0.4167}$$

$$I_{pu} = 0.4395 \angle -26.01^\circ \text{ pu}$$

$$[I_{actual}]_{Load} = I_{pu} * I_{Base} = (0.4395 \angle -26.01^\circ \text{ pu})(144.3 \text{ A})$$

$$[I_{actual}]_{Load} = I_{pu} * I_{Base} = 63.3 \angle -26.01^\circ \text{ A}$$

Reminder


The same **pu** current is running in the circuit. To get the **actual value** for the current we have to **select the right base** current

$$[I_{Base}]_1 = 72.2 \text{ A}$$

$$[I_{Base}]_2 = 36.2 \text{ A}$$


$$[I_{Base}]_3 = 144.3 \text{ A}$$

Example=4

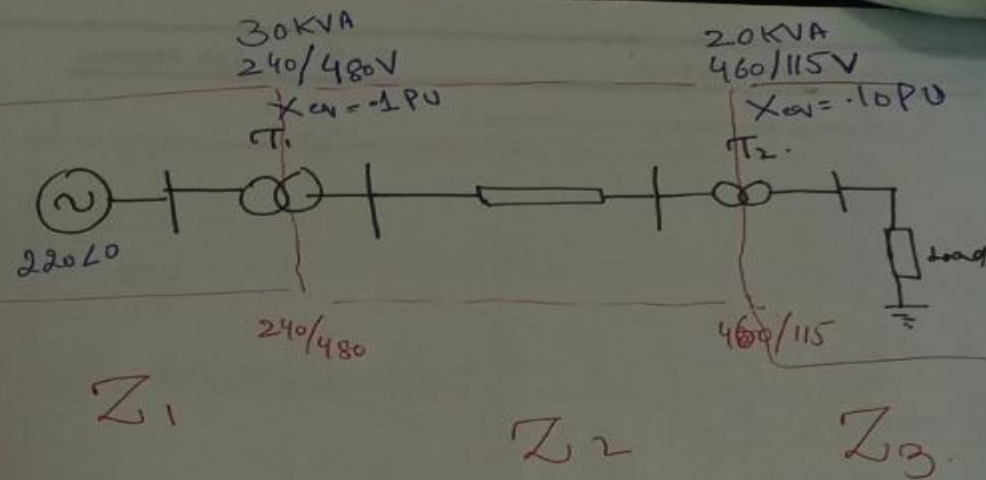

$$\Rightarrow \begin{cases} S_{\text{Base}} = 30\text{ KVA} \\ V_{\text{Base}} = 240\text{ V} \end{cases}$$

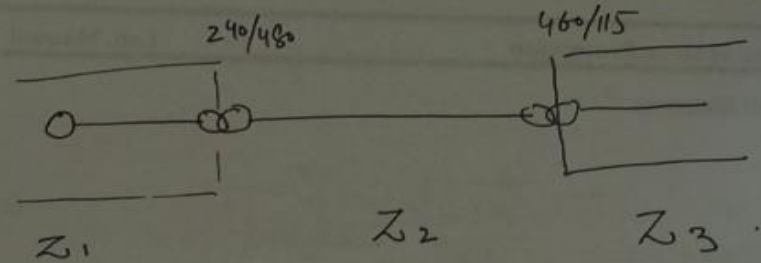- 2 $\begin{cases} \Rightarrow \text{Make Zones} \\ \Rightarrow S \text{ value Remain same} \end{cases}$
- $\Rightarrow \begin{cases} V \text{ will change} \\ \text{according to Zone} \end{cases}$
- $\Rightarrow \begin{cases} V \text{ will change} \\ \text{w.r.t turn Ratio of Transformer} \end{cases}$



$$\text{fix} \Rightarrow [S = 30 \text{ KVA}]$$

Voltage in 3 Zones $V_{\text{Base}} = 240$

Zone 1 :

$$\boxed{V_{\text{Base 1}} = 240} \quad \checkmark$$

Zone 2 :

$$V_{\text{Base 2}} = 240 \cdot \left[\frac{480}{240} \right]$$

$$\boxed{V_{\text{Base 2}} = 480} \quad \checkmark$$

$$\text{Zone 3 : - } V_{\text{Base 2}} \left[\frac{115}{460} \right]$$

$$= 480 \left[\frac{115}{460} \right]$$

$$\boxed{V_{\text{Base 3}} = 120 \text{ V}} \quad \checkmark$$

Impedance Base in Zones

Zone 1 :-

$$\begin{aligned} [Z_{Base}]_1 &= \frac{V_{Base 1}^2}{S_{Base 1}} \\ &= \frac{240^2}{30K} = 1.92 \Omega \end{aligned}$$

Zone 2 :-

$$\begin{aligned} [Z_{Base}]_2 &= \frac{[V_{Base 2}]^2}{S_{Base 2}} \\ &= \frac{480^2}{30K} = 7.68 \Omega \end{aligned}$$

Zone 3 :-

$$\begin{aligned} [Z_{Base}]_3 &= \frac{[V_{Base 3}]^2}{S_{Base 3}} \\ &= \frac{120^2}{30K} = 0.48 \Omega \end{aligned}$$

Per unit value:-

Zone 1:-

$$V_{Source\ pu} = \frac{V_{Source}}{V_{pu}} = \frac{220}{220} \angle 0$$

$$\checkmark V_{Source\ pu} = 1 \angle 0 \text{ pu}$$

Zone 2:-

$$X_{line} = 2 \Omega$$

$$X_{line\ pu} = \frac{X_{line}}{Z_{base2}} = \frac{2}{7.68}$$

$$\checkmark X_{line\ pu} = 0.26 \text{ pu}$$

$$X_{\pi1} = X_{pold} \cdot \frac{S_{new}}{S_{old}} \cdot \frac{V_{old}^2}{V_{new}^2}$$
$$= 1 \cdot \frac{30k}{30k} \cdot \frac{480^2}{480^2}$$

$$\checkmark X_{\pi1} = 1 \text{ pu}$$

Zone 3 :-

$$X_{T2} = X_{Tdel} \cdot \frac{S_{new}}{S_{old}} \cdot \frac{[V_{old base}]^2}{[V_{new old}]^2}$$
$$= .1 \cdot \frac{30K}{20K} \cdot \frac{115^2}{120^2}$$

$$X_{T2} p_0 = -1378 p_0$$

$$Z_{load} = .9 + j.2$$

$$\{Z_{base}\}_3 = .48 \sqrt{2}$$


$$Z_{load p_0} = \frac{.9 + j.2}{.48}$$

$$\{Z_{load}\}_{p_0} = 1.87 + j.4167$$

p.u.

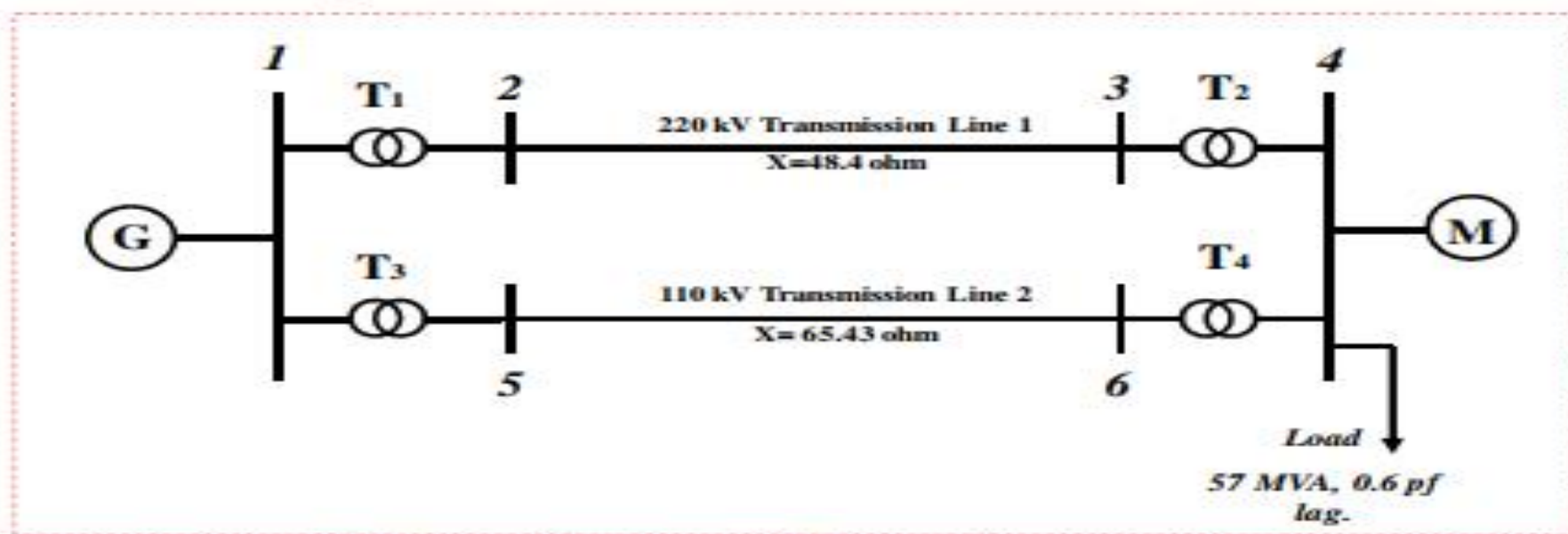Example 5:

The single-line diagram of a three phase power system is shown in the Figure. Select a common base of 100 MVA and 22 kV on the generator side.




1. Draw an impedance diagram of the system.

Think about this:

What are the Voltage and Power bases?

Make sure that the base voltages in the system zones are related by the turns ratios of the intervening transformers.

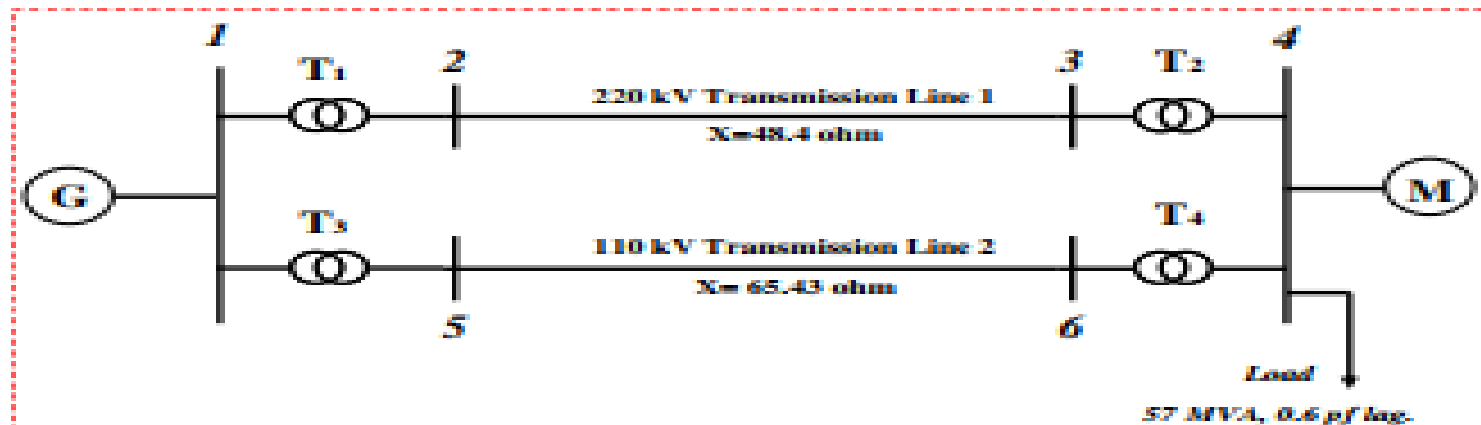How many zones do we have in this system?




Do we have impedances in pu, % or in ohms?

Is there any difference between system voltages and selected bases?

Is there any difference between system Rated MVA and Base MVA?

Is there any difference between system Rated kV and Operating kV?

	MVA	Voltage	X
G	90	22 kV	18 %
T1	50	22/220 kV	10 %
T2	40	220/11 kV	06 %
T3	40	22/110 kV	6.4 %
T4	40	110/11 kV	08 %
M	66.5	10.45kV kV	18.5 %

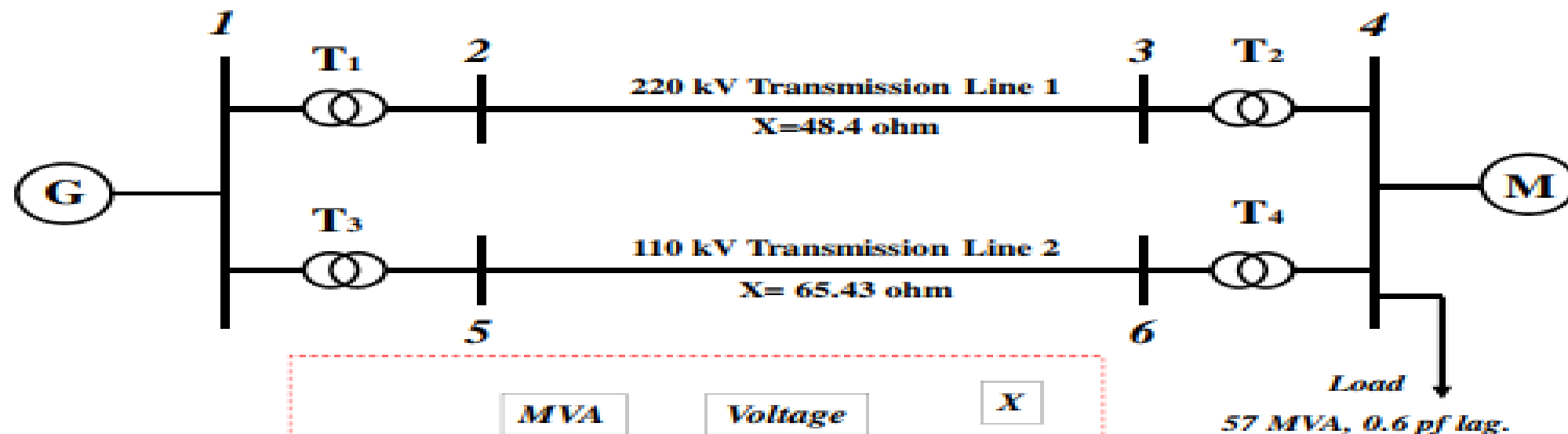

	MVA	Voltage	X
G	90	22 kV	18 %
T1	50	22/220 kV	10 %
T2	40	220/11 kV	06 %
T3	40	22/110 kV	6.4 %
T4	40	110/11 kV	08 %
M	66.5	10.45kV	18.5 %


Note:
X% is calculated according to MVA and kV of each part of the network.

Solution:

The base voltages in the system zones are related by the turns ratios of the transformers.

Voltage bases must be determined for all sections of the network.
A common base of **100 MVA** and **22 kV** on the generator side is selected.

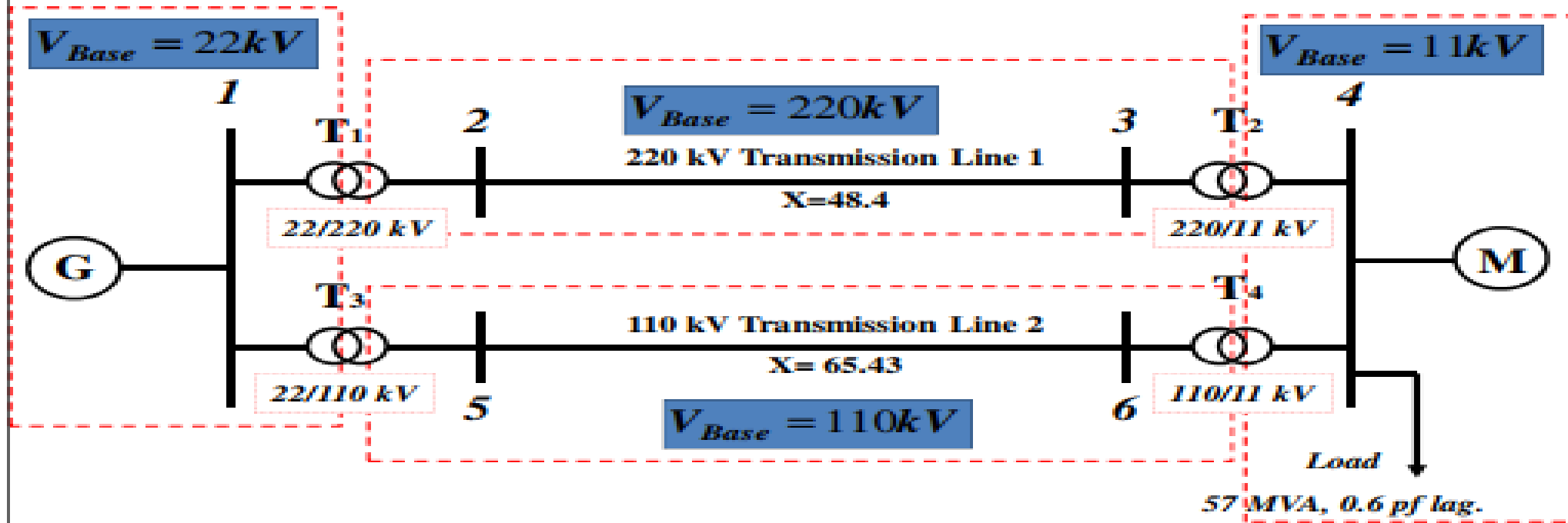
The voltage levels that exist in the system are 11kV, 22kV, 110kV and 220kV. Select the voltage bases as:



For transformers and generator

$$(Z_{p.u.})_{new} = (Z_{p.u.})_{old} \frac{|(S_{Base})_{new}|}{|(S_{Base})_{old}|} \cdot \frac{|(V_{Base})_{old}|^2}{|(V_{Base})_{new}|^2} \text{ p.u.}$$

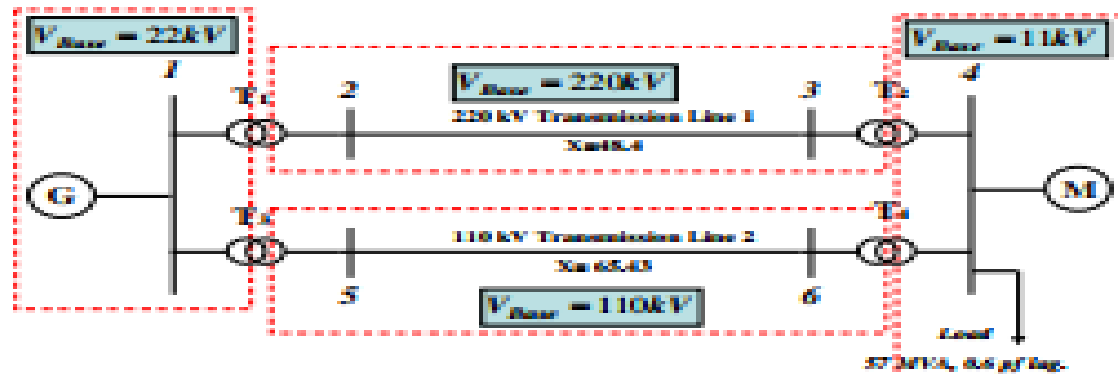Since the *volt bases* are the same for transformers and generator, then



$$(Z_{p.u.})_{new} = (Z_{p.u.})_{old} \frac{|(S_{Base})_{new}|}{|(S_{Base})_{old}|}$$

$$X_G = 0.18 \frac{100}{90} = 0.20 \text{ pu}$$

$$X_{T1} = 0.10 \frac{100}{50} = 0.20 \text{ pu}$$

$$X_{T2} = 0.06 \frac{100}{40} = 0.15 \text{ pu}$$

$$X_{T3} = 0.064 \frac{100}{40} = 0.16 \text{ pu}$$

$$X_{T4} = 0.08 \frac{100}{40} = 0.20 \text{ pu}$$


	MVA	Voltage	X
G	90	22 kV	18 %
T1	50	22/220 kV	10 %
T2	40	220/11 kV	06 %
T3	40	22/110 kV	6.4 %
T4	40	110/11 kV	08 %

For the motor

	<i>MVA</i>	<i>Voltage</i>	<i>X</i>
<i>M</i>	66.5	10.45kV	18.5 %

$$(Z_{p.u.})_{new} = (Z_{p.u.})_{old} \frac{|(S_{Base})_{new}|}{|(S_{Base})_{old}|} \cdot \frac{|(V_{Base})_{old}|^2}{|(V_{Base})_{new}|^2} \text{ p.u.}$$
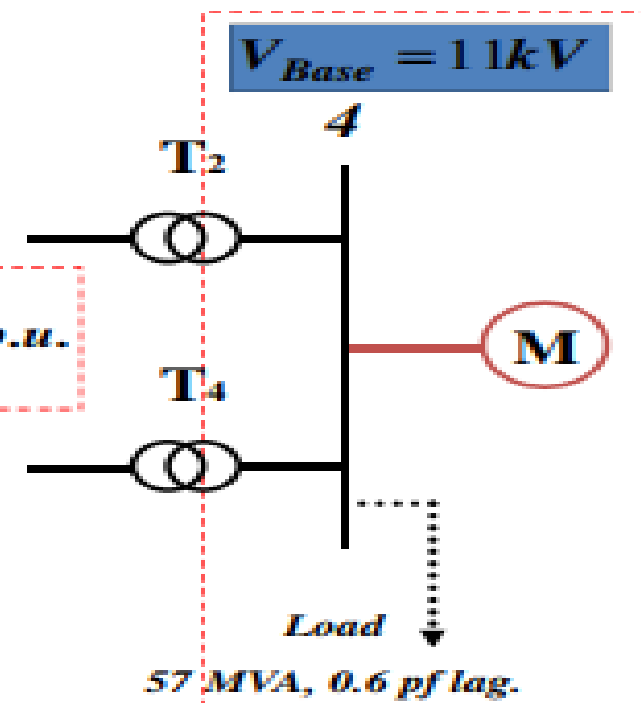
$$X_M = 0.185 \frac{100}{66.5} \left(\frac{10.45}{11} \right)^2 = 0.25 \text{ pu}$$



For the Transmission Lines

$$X_{\text{Line 1}} = 48.4 \text{ ohm}$$

$$X_{\text{Line 2}} = 65.43 \text{ ohm}$$


$$Z_{p.u.} = \frac{Z_{\Omega}}{Z_{Base}}$$

$$|Z_{Base}| = \frac{|V_{Base}|^2}{|S_{base}|}$$

$$Z_{p.u.} = \frac{Z_{\Omega} [MVA, S_{Base}]}{[kV, V_{Base}]^2} p.u.$$

$$X_{line 1} = \frac{48.4(100)}{(220)^2} = 0.10 p.u.$$
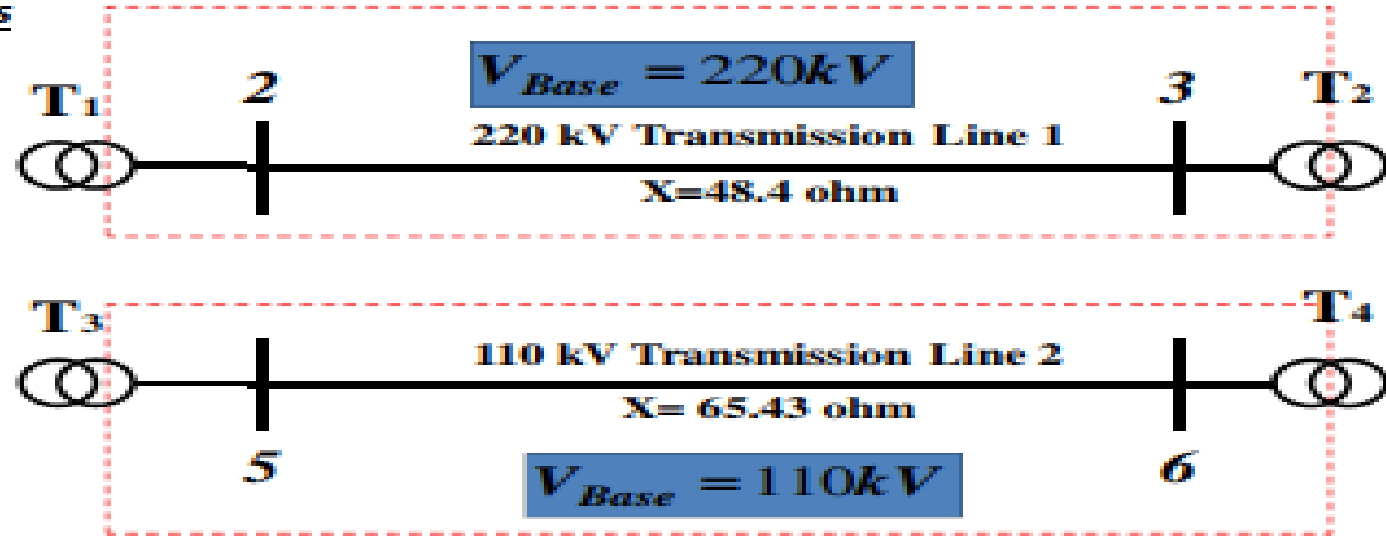
$$X_{line 2} = \frac{65.43(100)}{(110)^2} = 0.54 p.u.$$



For the Load

Load = 57 MVA, 0.6 pf lag.

$$S_{3\phi} = \sqrt{3}(V_{LL})(I_L)^* = \sqrt{3}(V_{LL})\left(\frac{V_{\phi}}{(Z_L)}\right)^*$$


$$= \sqrt{3}(V_{LL})\left(\frac{V_{LL}}{(\sqrt{3}Z_L)}\right)^* = \frac{|V_{LL}|^2}{Z_L^*}$$

$$Z_{Load} = \frac{(V_{L-L})^2}{S_{L(3\phi)}^*} \text{ ohm}$$

$$S_{L(3\phi)} = 57 \angle 53.13 \text{ MVA} \quad V_{L-L} = 10.45 \text{ kV}$$



$$Z_{Load} = \frac{(10.45)^2}{57 \angle -53.13} = 1.1495 + j1.53267 \text{ ohm}$$
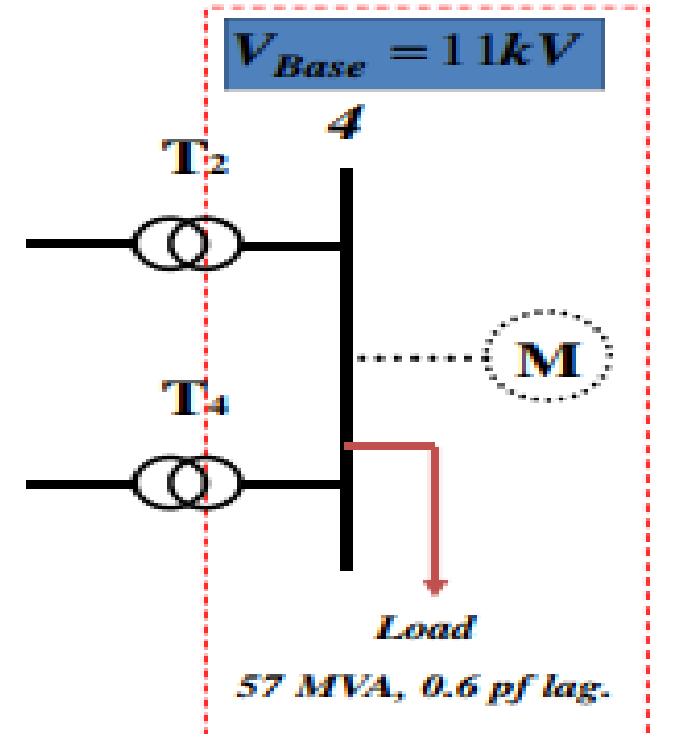
$$(Z_{Load})_{pu} = \frac{Z_{Load} (MVA, 100)}{(kV, 11)^2} = 0.95 + j1.2667 \text{ p.u.}$$



$$Z_{p.u.} = \frac{Z_{\Omega} \text{ MVA, } S_{Base}}{1 \text{ kV, } V_{Base}^2} \text{ p.u.}$$

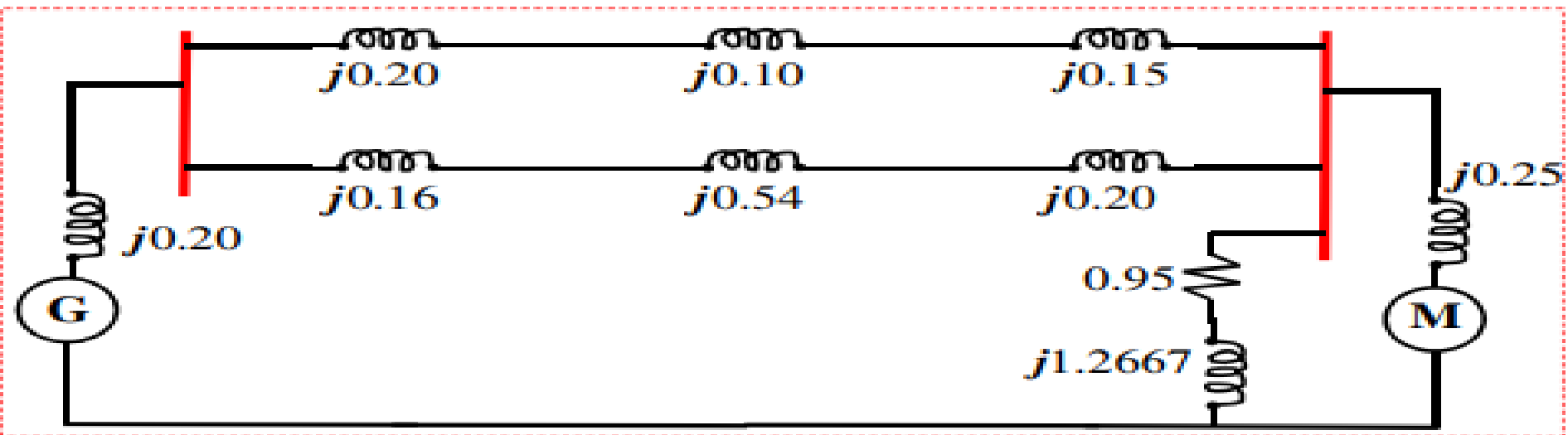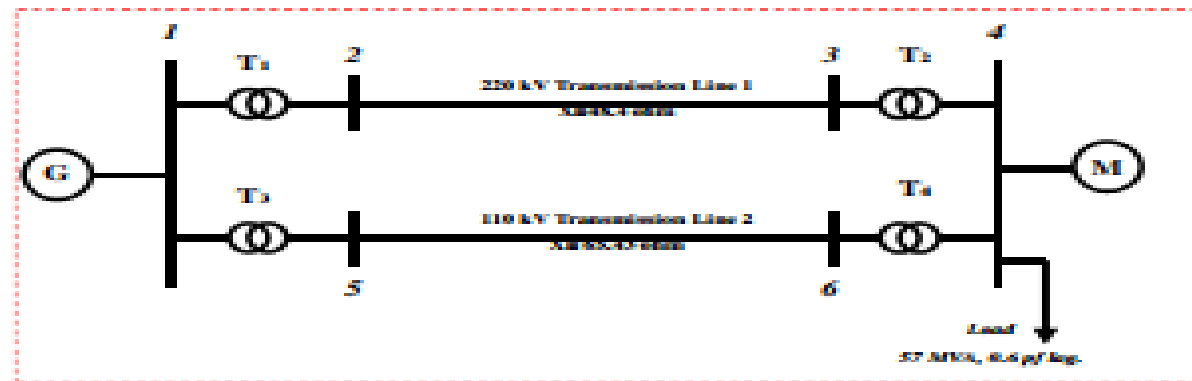
1. The per unit impedance diagram of the system is:



S for VL

Example 5
portion for
static load

⇒ Static load is
mostly Y-Connected.

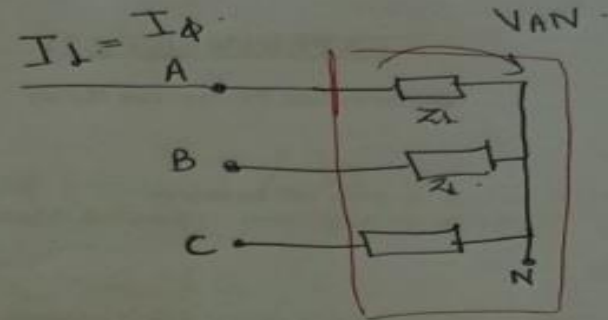

57 MVA - 0.6 pf lag.

$$S_{3\phi} = 3 V_{\phi} I_{\phi}^*$$

$$I_{\phi} = \frac{V_{\phi}}{Z_L}$$

$$V_L = \sqrt{3} V_{\phi}$$

$$= 3 \cdot \frac{V_L}{\sqrt{3}} I_{\phi}^*$$

$$= \sqrt{3} \frac{V_L}{\cancel{\sqrt{3}}} \left(\frac{V_{\phi}}{Z_L} \right)^*$$

$$= \sqrt{3} V_L \cdot \frac{V_L}{\sqrt{3} Z_L^*}$$

$$S_{3\phi} = \frac{(V_L)^2}{Z_L^*}$$

$$Z_{\text{Load}} = \frac{(V_{L-L})^2}{S_{L(3\phi)}^*}$$

$$S_{L(3\phi)} = 57 \angle 53.13 \text{ MVA}$$


$$V_{L-L} = 10.45 \text{ KV}$$

$$Z_{\text{Load}} = \frac{(10.45)^2}{57 \angle -53.13} = 1.149 + j1.5 \Omega$$


$$Z_{\text{Load PU}} = \frac{Z_{\text{Load}} \cdot S}{V^2}$$

$$Z_{\text{Load PU}} = \frac{Z_{\text{Load}} \cdot 100 \text{ MVA}}{11^2} = .95 + j1.2 \text{ PU}$$

Zones in
Example 5

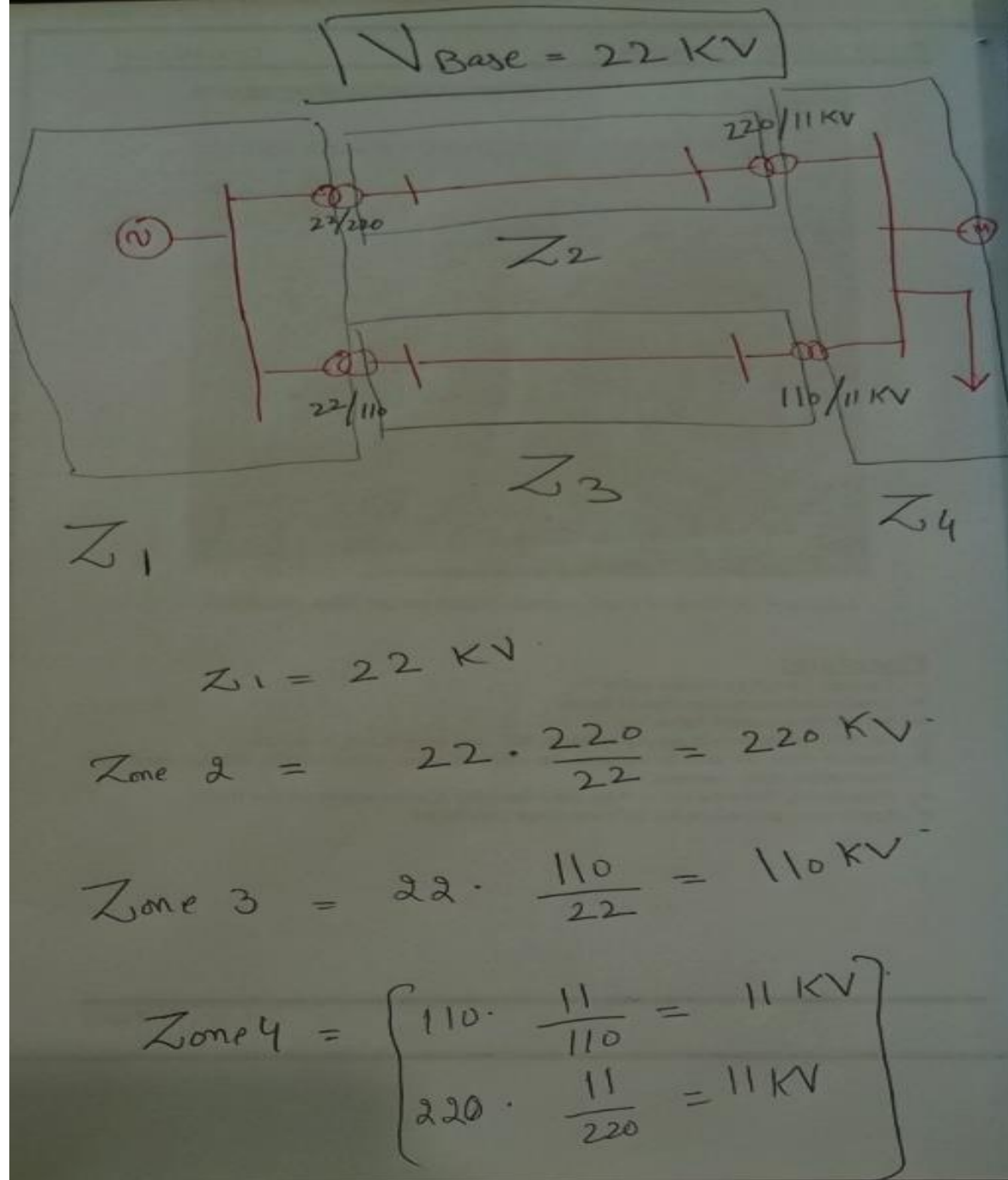

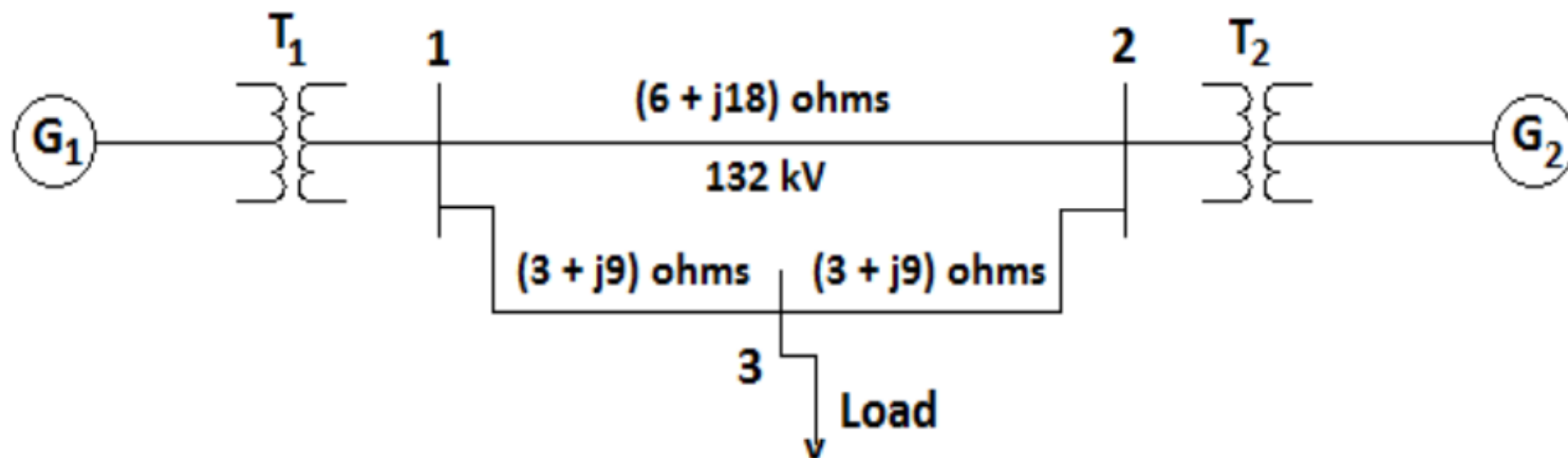A single line diagram of a single phase circuit is shown in Fig. 1. Draw the per unit impedance diagram assuming the base values of 100 MVA and 100 kV in the transmission line sections.



The Generators and Transformers are rated as follows:


Generator 1:	50 MVA,	12.2 kV,	$X'' = 0.20$ pu
Generator 2:	25 MVA,	13.8 kV,	$X'' = 0.15$ pu
Transformer 1:	80 MVA,	12.2/132 kV,	$X = 10\%$
Transformer 2:	100 MVA,	13.8/132 kV,	$X = 15\%$
Load:	60 MVA,	0.8 pf lagging at 124 kV	

Solution:-

Base Value in Transmission Line Zone

$$S_b = 100 \text{ MVA}$$

$$V_b = 100 \text{ KV}$$

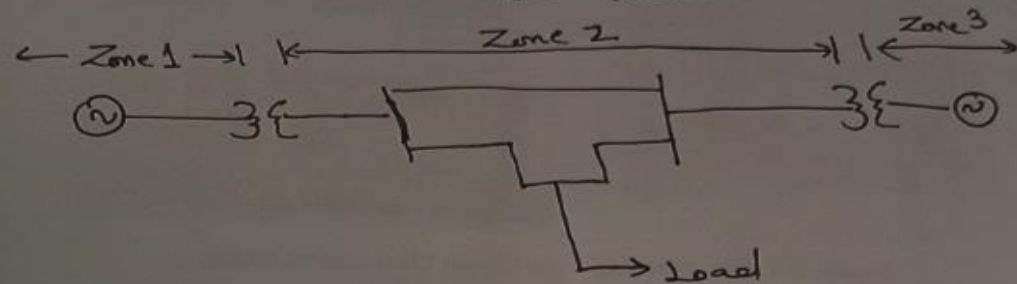

Zone 1 :-

$$S_b = 100 \text{ MVA}$$

$$V_b = 100 \times \frac{12.2}{13.2} = 9.24 \text{ KV}$$

$$X_{G1} = 0.2 \times \frac{12.2^2}{9.24^2} \times \frac{100}{50} = j.697 \text{ pu}$$

$$X_{T1} = 0.10 \times \frac{12.2^2}{9.24^2} \times \frac{100}{80} = j.2179 \text{ pu}$$

The Generators and Transformers are rated as follows:


Generator 1: 50 MVA, 12.2 kV, $X'' = 0.20 \text{ pu}$

Generator 2: 25 MVA, 13.8 kV, $X'' = 0.15 \text{ pu}$

Transformer 1: 80 MVA, 12.2/132 kV, $X = 10 \%$

Transformer 2: 100 MVA, 13.8/132 kV, $X = 15\%$

Load: 60 MVA, 0.8 pf lagging at 124 kV

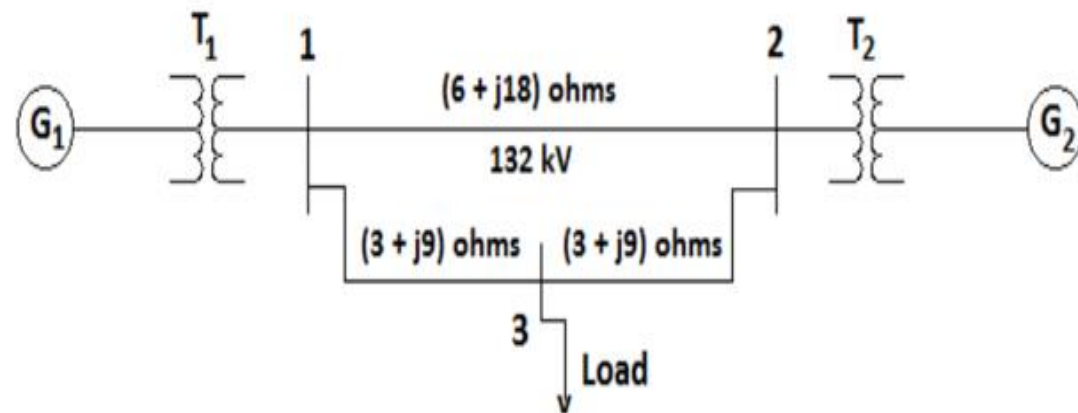

Zone 2:

$$S_b = 100 \text{ MVA}$$

$$V_b = 100 \text{ kV}$$

$$Z_{\text{line}_1} = \frac{6 + j18}{100^2} \times 100 = .06 + j.18 \text{ pu}$$

$$Z_{\text{line}_2} = .03 + j.09 \text{ pu} + .03 + j.09 \text{ pu}$$

$$S_{\text{load}} = 60 (\cos \alpha + j \sin \alpha)$$

$$= 60 (.8 + j.6)$$

$$S_{\text{load}} = 48 + j36 \text{ MVA}$$

$$Z_{\text{load}} = \frac{124^2}{48 - j36}$$

$$= 205 + j153.7 \Omega$$

$$Z_{\text{pu}} = \frac{205 + j153.7}{100^2} \cdot 100 = 2.05 + j1.53$$

$$Z_{\text{pu}} = 2.05 + j1.53 \text{ pu}$$

The Generators and Transformers are rated as follows:


Generator 1: 50 MVA, 12.2 kV, $X'' = 0.20 \text{ pu}$

Generator 2: 25 MVA, 13.8 kV, $X'' = 0.15 \text{ pu}$

Transformer 1: 80 MVA, 12.2/132 kV, $X = 10 \%$

Transformer 2: 100 MVA, 13.8/132 kV, $X = 15 \%$

Load: 60 MVA, 0.8 pf lagging at 124 kV

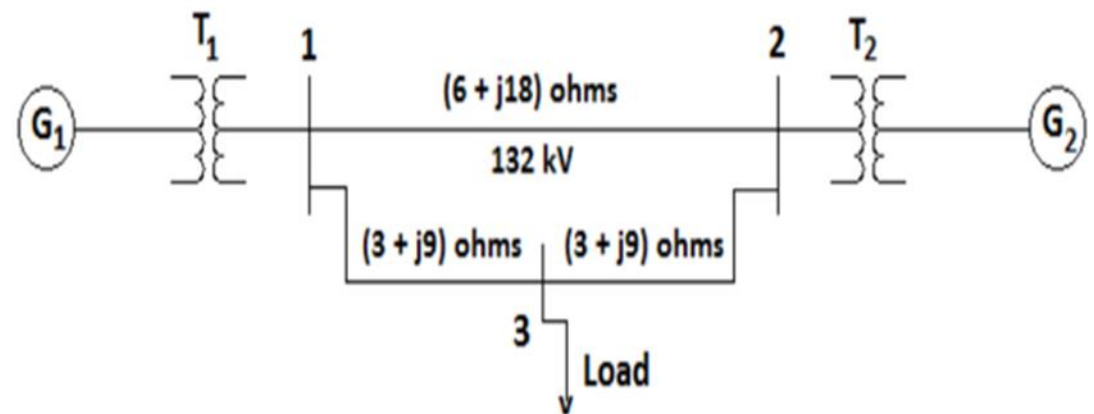

Zone 3:-

$$S_b = 100 \text{ MVA}$$

$$V_b = 100 \times \frac{13.8}{132} = 10.45 \text{ kV}$$

$$X_{G1} = .15 \times \frac{13.8^2}{10.45^2} \times \frac{100}{25} = j1.046 \text{ pu}$$

$$X_{T2} = .15 \times \frac{13.8^2}{10.45^2} \times \frac{100}{100} = j.262 \text{ pu}$$

The Generators and Transformers are rated as follows:

Generator 1: 50 MVA, 12.2 kV, $X'' = 0.20 \text{ pu}$

Generator 2: 25 MVA, 13.8 kV, $X'' = 0.15 \text{ pu}$

Transformer 1: 80 MVA, 12.2/132 kV, $X = 10 \%$

Transformer 2: 100 MVA, 13.8/132 kV, $X = 15\%$

Load: 60 MVA, 0.8 pf lagging at 124 kV

