

PSA_1

Power System Basics

- All power systems have three major components: Generation, Load and Transmission.
- Generation: Creates electric power.
- Load: Consumes electric power.
- Transmission: Transmits electric power from generation to load.

Power system



Generation




Transmission



Loads


Power system

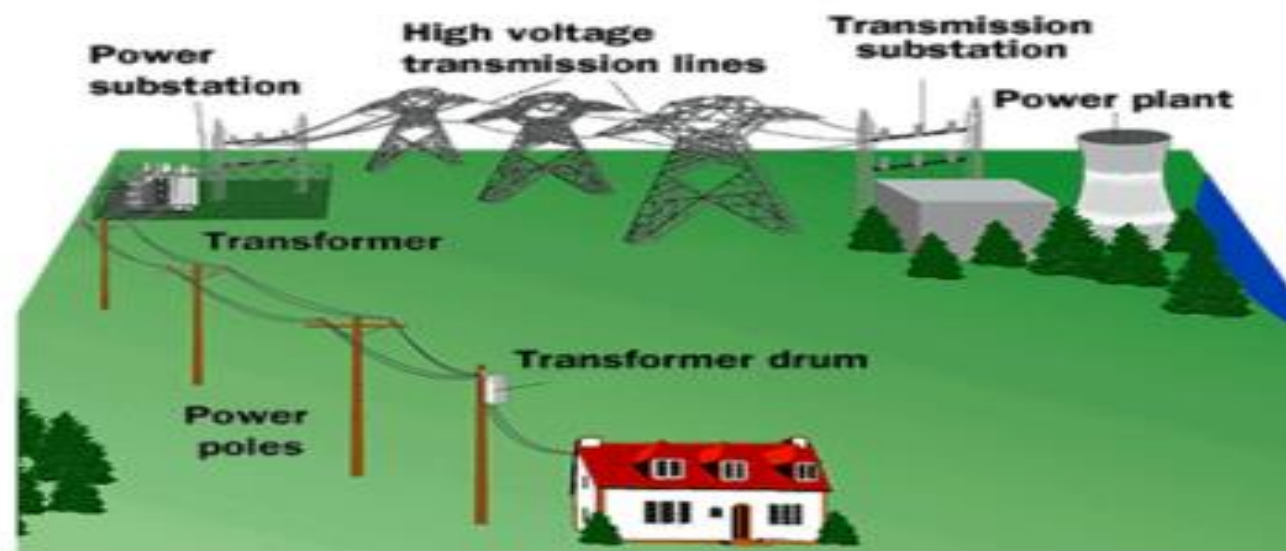


One-line Diagram

- ❑ Most power systems are balanced three phase systems.
- ❑ A balanced three phase system can be modeled as a single (or one) line.
- ❑ One-lines show the major power system components, such as generators, loads, transmission lines.
- ❑ Components join together at a bus.


Example One-Line Diagram

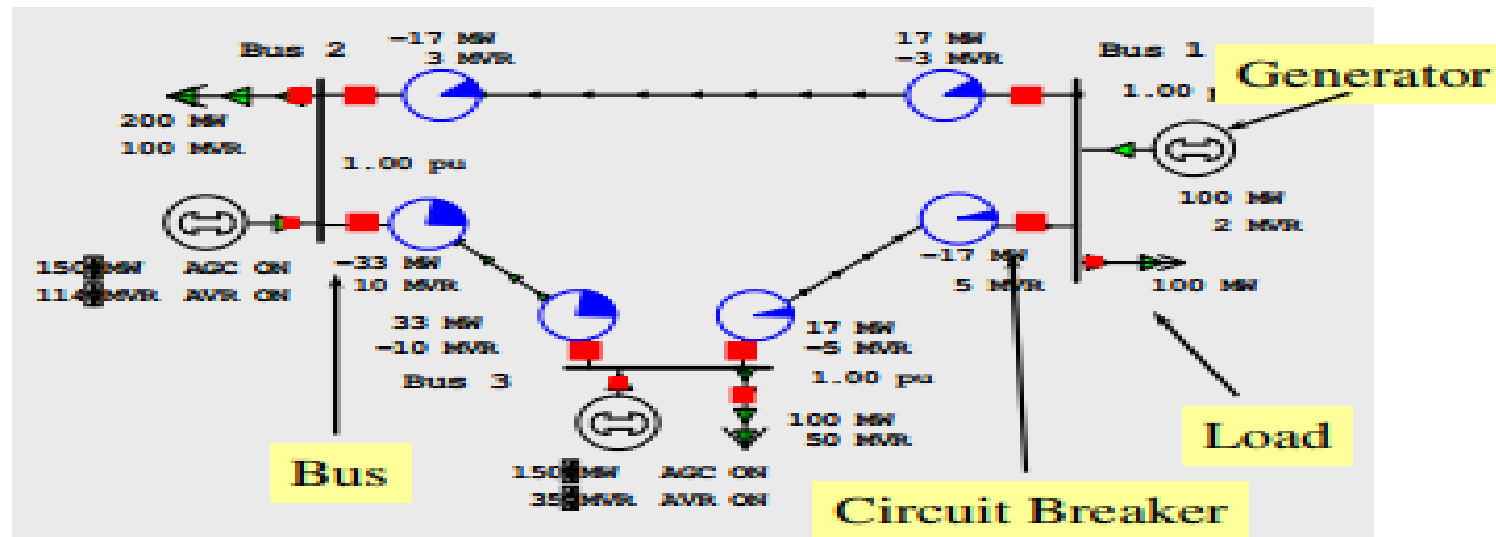

CHARACTERISTICS OF STEAM UNITS

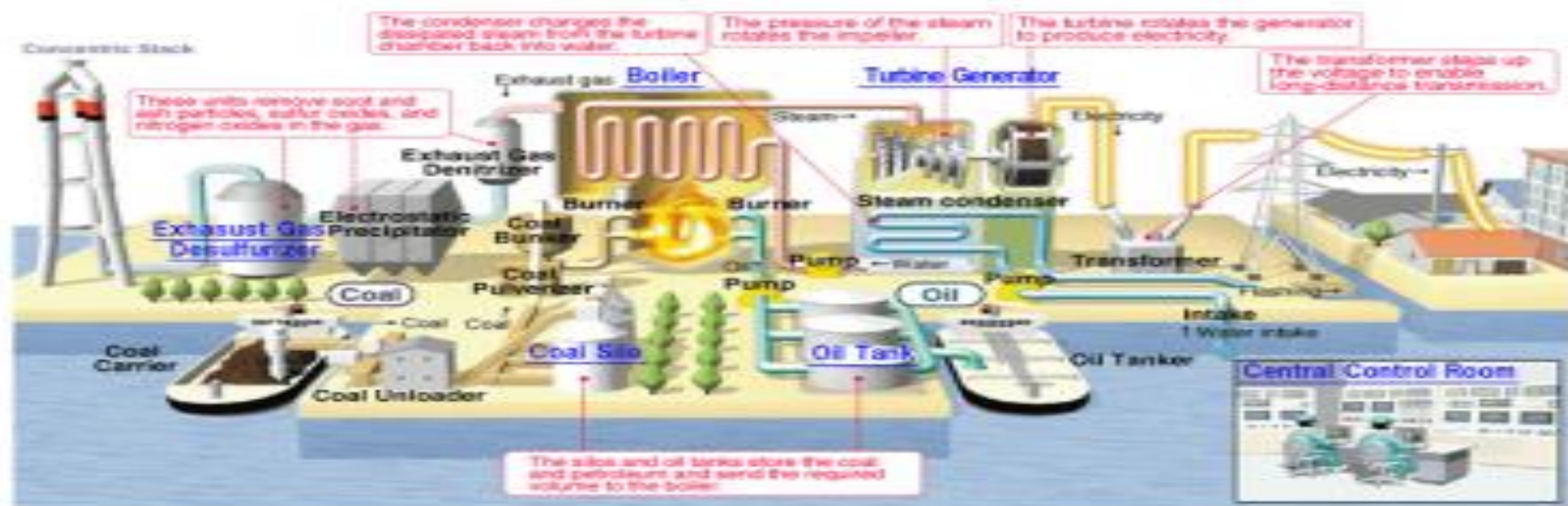

CHARACTERISTICS OF COMBINED CYCLE UNITS

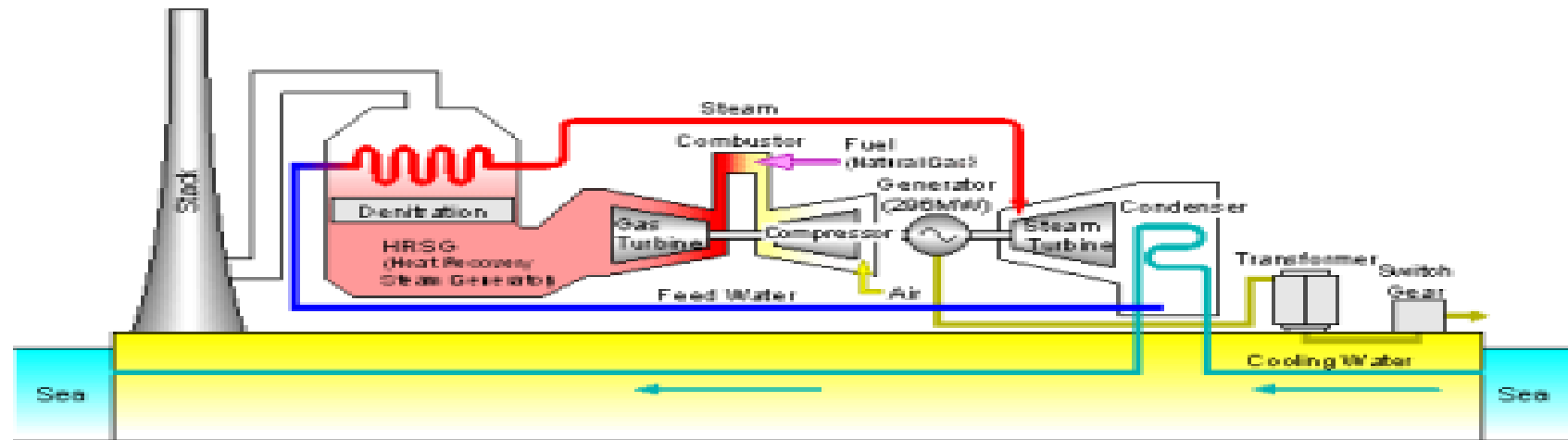

Loads

- Can range in size from less than a single watt to 10's of MW.
- Loads are usually aggregated.
- The aggregate load changes with time, with strong daily, weekly and seasonal cycles.

Transmission

- Goal is to move electric power from generation to load with as low of losses and cost as possible.
- $P \propto V I$ or $P/V \propto I$
- Losses are $3 \cdot I^2 R$ (for three phase)
- Less losses at higher voltages, but more costly to construct and insulate.

Transmission



500 kV transmission line



132 kV transmission line




69 kV transmission line

Transmission and Distribution

- Typical high voltage transmission voltages are 500, 345, 230, 161, 138 and 69 kV.
- Transmission tends to be a grid system, so each bus is supplied from two or more directions.
- Lower voltage lines are used for distribution, with a typical voltages of 13.8, 11 and 6.6 kV.

Complex Number :

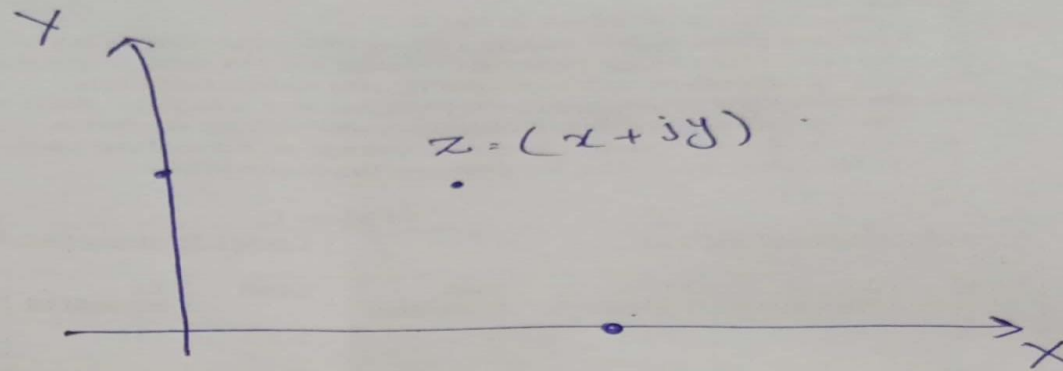

$$Z = x + jy$$

$$|Z| = \sqrt{x^2 + y^2}$$

$$\theta = \tan^{-1}\left(\frac{y}{x}\right)$$

$$Z = |Z| \angle \theta$$

$$V = |V| \angle \theta$$


$$I = |I| \angle \theta$$

S = Apparent Power
 P = ~~Complex~~ Real Power
 Q = Reactive Power.

$$S = P + jQ$$





$$P = VI \cos \phi$$

$$Q = VI \sin \phi$$

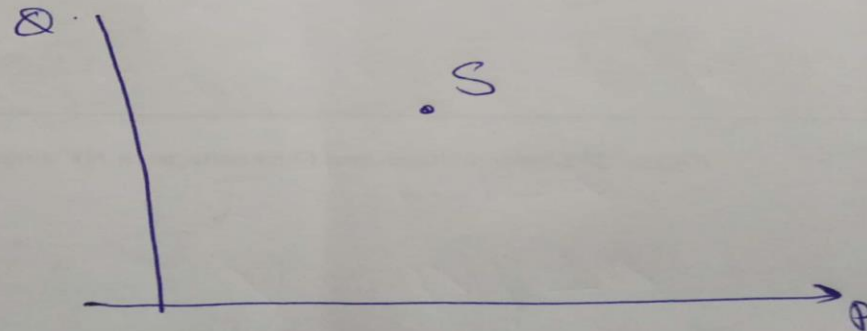

$$V = V \angle \phi_v$$

$$I = I \angle \phi_i$$

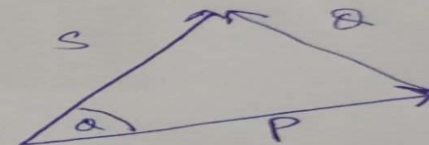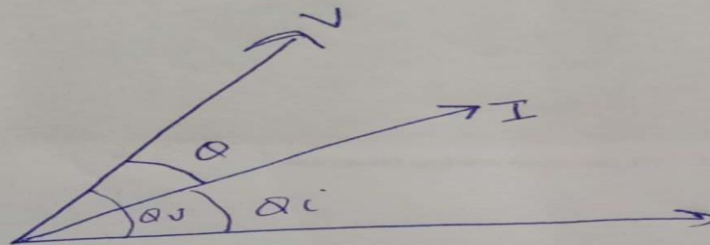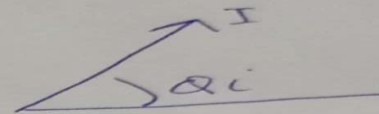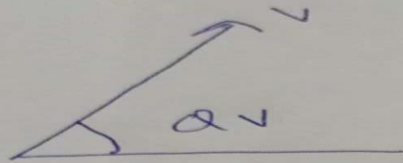

$$S = VI^*$$

$$= V I \angle \phi_v - \phi_i$$


$$S = V I \angle \theta$$

$$S = \cancel{V/I} \cos \phi + jVI \sin \phi$$

$$S = VI^* = P + jQ$$

$$|S| = \sqrt{P^2 + Q^2}$$

Electric Power Delivery Efficiency

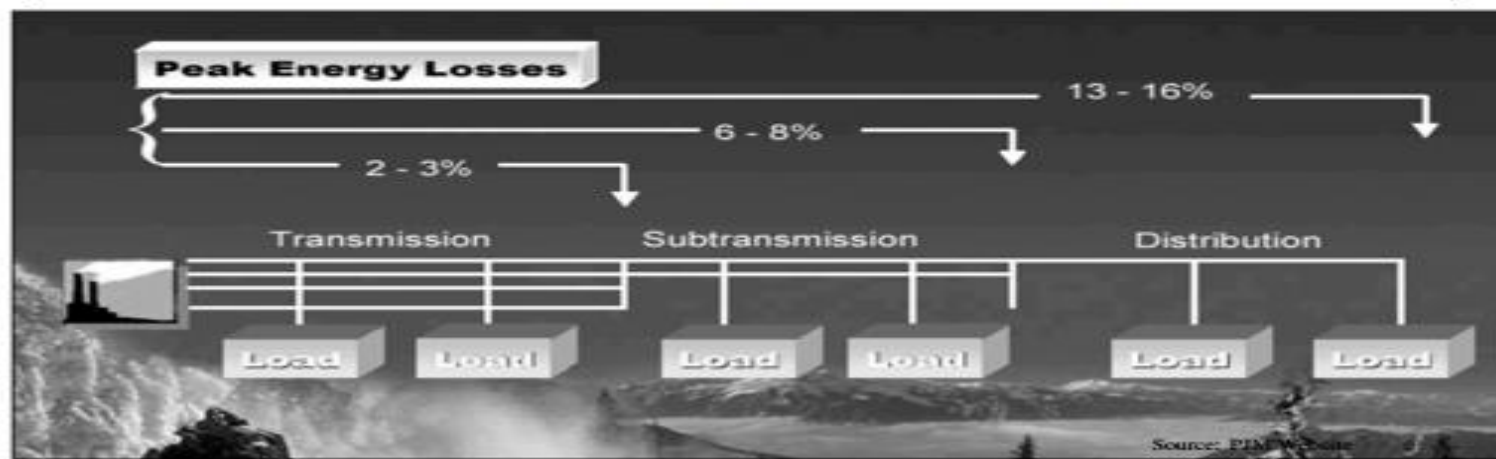

Power Balance Constraints

- Power flow refers to how the power is moving through the system.
- At all times the total power flowing into any bus MUST be zero!
- This is known as Kirchhoff's law. And it can not be repealed or modified.
- Power is lost in the transmission system.


Basic Power Control

- Opening a circuit breaker causes the power flow to instantaneously(nearly) change.
- No other way to directly control power flow in a transmission line.
- By changing generation we can indirectly change this flow.

Transmission Line Limits

- Power flow in transmission line is limited by a number of considerations.
- Losses ($I^2 R$) can heat up the line, causing it to sag. This gives line an upper thermal limit.
- Thermal limits depend upon ambient conditions. Many utilities use winter/summer limits.

Overloaded Transmission Line

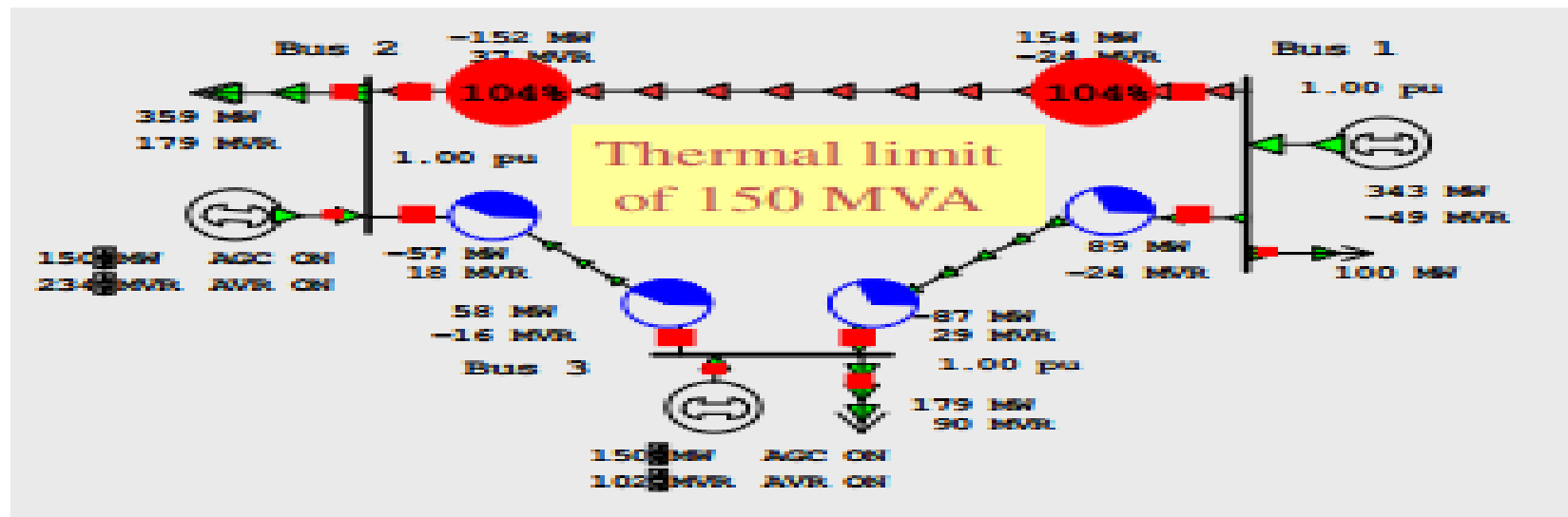

Reactive Power

- Reactive power is supplied by:
 - generators
 - capacitors
 - transmission lines
 - loads
- Reactive power is consumed by
 - loads
 - transmission lines and transformers

Voltage Magnitude

- Power systems must supply electric power within a narrow voltage range, typically with 5% of a nominal value.
- For example, wall outlet should supply 220 volts, with an acceptable range from 209 to 231 volts.
- Voltage regulation is a vital part of system operations.

Balanced Three-phase Circuits


Wye-Connected System

- ❑ The neutral point is grounded
- ❑ The three-phase voltages have equal magnitude.
- ❑ The phase-shift between the voltages is 120 degrees.

$$V_{an} = |V| \angle 0^\circ = V$$

$$V_{bn} = |V| \angle -120^\circ$$

$$V_{cn} = |V| \angle -240^\circ$$

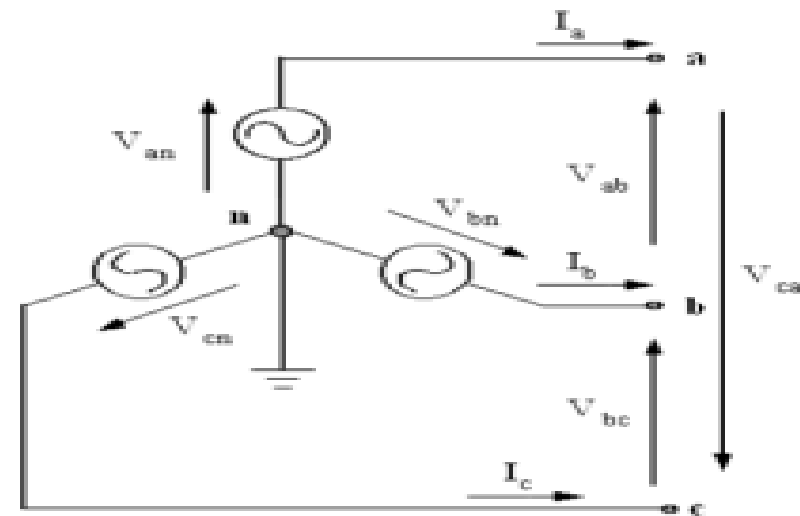

Balanced Y-Connections


Wye-Connected System

- Line-to-line voltages are the difference of the phase voltages

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3} V \angle 30^\circ$$


$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V \angle -90^\circ$$
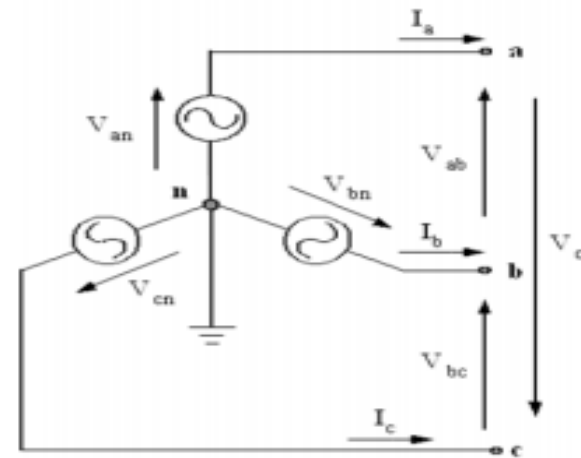
$$V_{ca} = V_{cn} - V_{an} = \sqrt{3} V \angle 150^\circ$$





Balanced Y-Connections

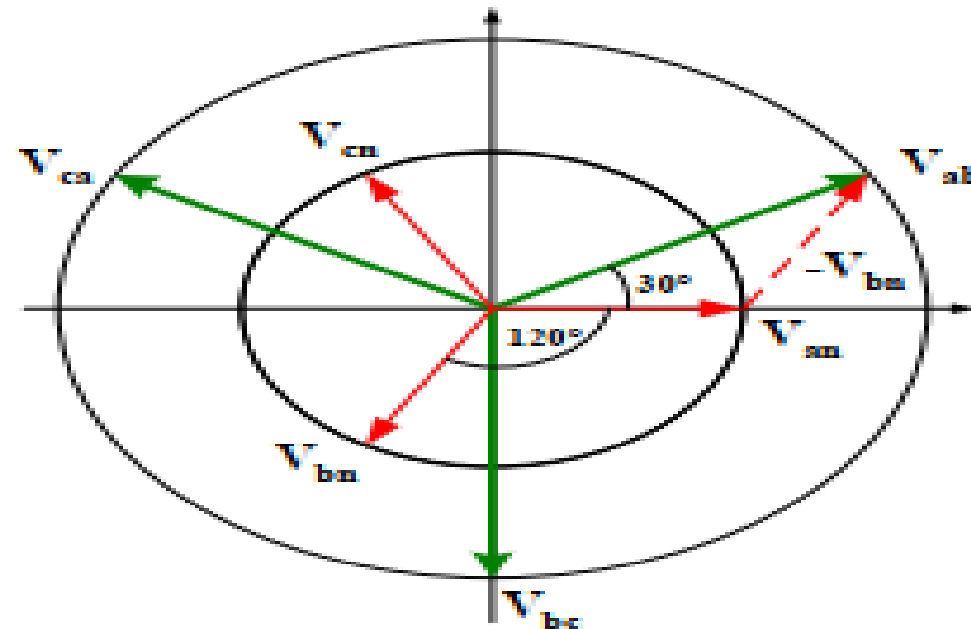- Phasor diagram is used to visualize the system voltages
- Wye system has two type of voltages: Line-to-neutral, and line-to-line.
- The line-to-neutral voltages are shifted with 120°
- The line-to-line voltage leads the line to neutral voltage with 30°
- The line-to-line voltage is $\sqrt{3}$ times the line-to-neutral voltage.


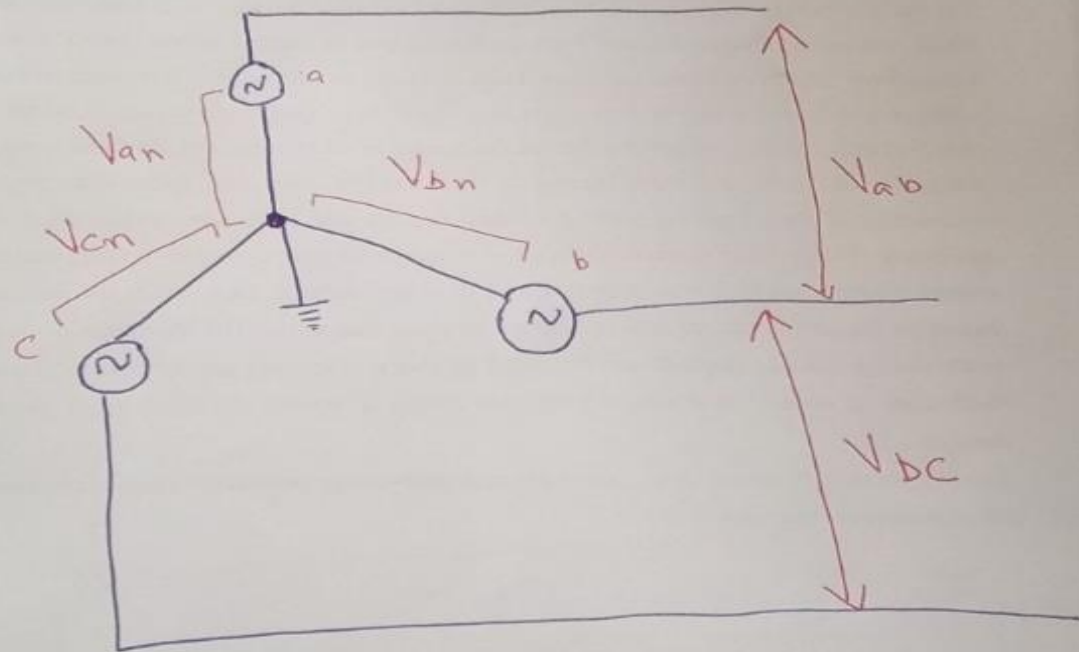
$$V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_p \angle 30^\circ$$



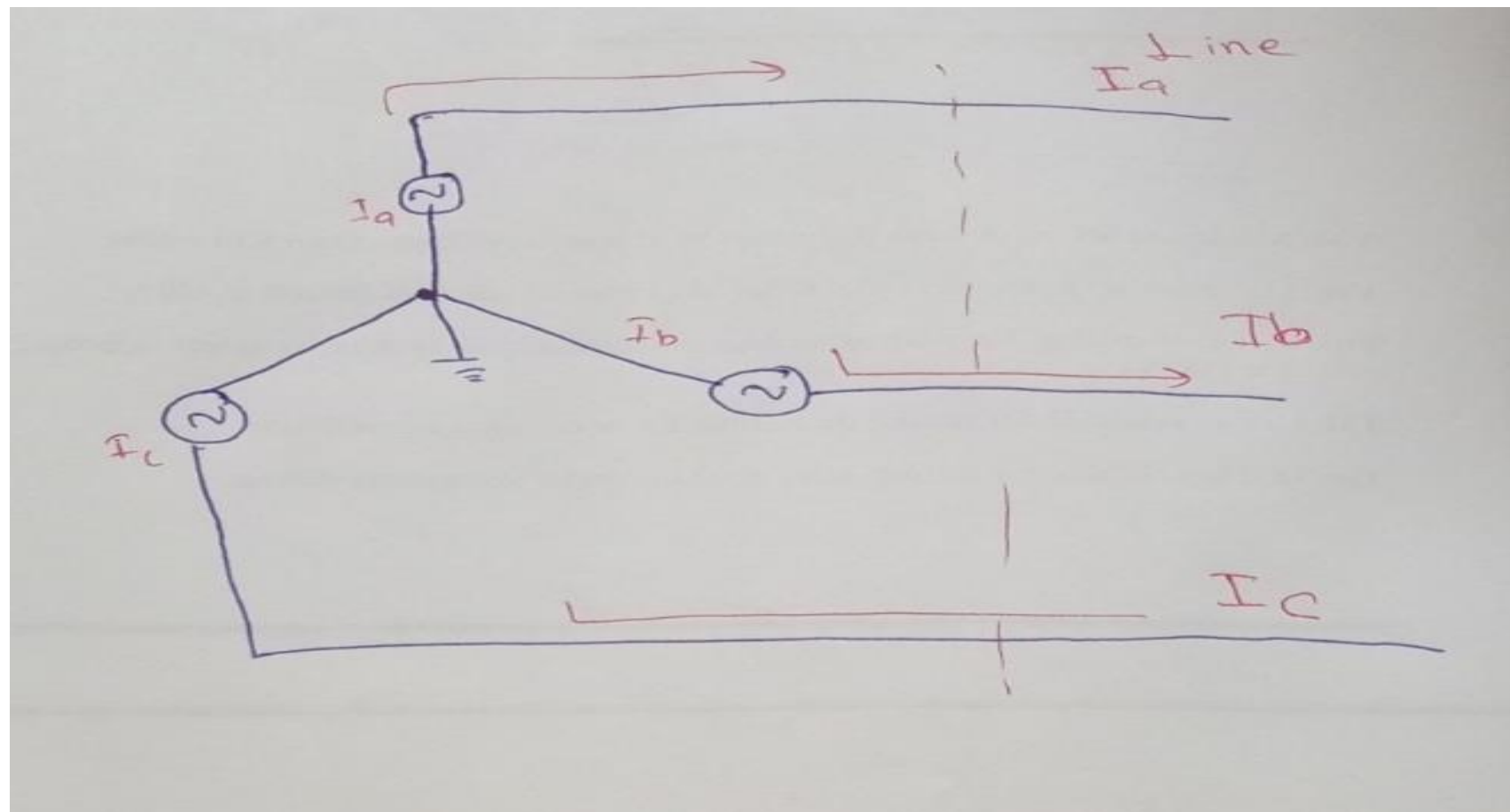


Balanced Y-Connections

Y-Connected Loaded System

- The load is a balanced and each one = Z
- Each phase voltage drives current through the load.
- The phase current expressions are:

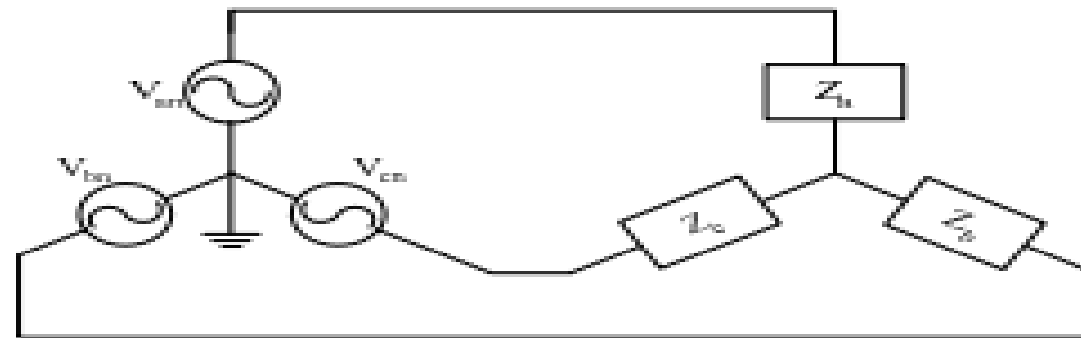
$$I_a = \frac{V_{an}}{Z}, \quad I_b = \frac{V_{bn}}{Z}, \quad I_c = \frac{V_{cn}}{Z}$$



Balanced Y-Connections

Wye-Connected Loaded System

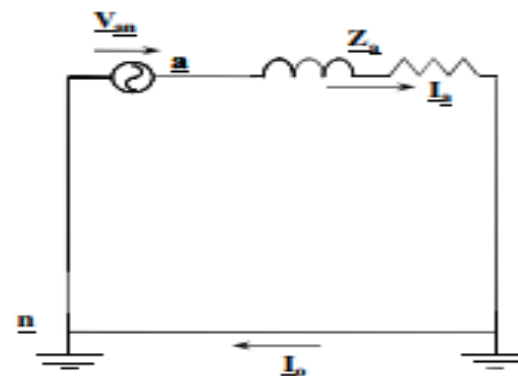- Since the load is balanced ($Z_a = Z_b = Z_c$) then: Neutral current = 0
- This case single phase equivalent circuit can be used (phase a, for instance, only).
- Phase b and c are eliminated.



Balanced Y-Connections

Wye-Connected System with balanced load


- A single-phase equivalent circuit is used
- Only phase a is drawn, because the magnitude of currents and voltages are the same in each phase. Only the phase angles are different (-120° phase shift)
- The supply voltage is the line to neutral voltage.
- The single phase loads are connected to neutral or ground.



Balanced Δ Loads

- The system has only one voltage : the line-to-line voltage ()
- The system has two currents : V_{LL}
 - line current
 - phase current
- The phase currents are:

$$I = \frac{V_{ab}}{Z}$$

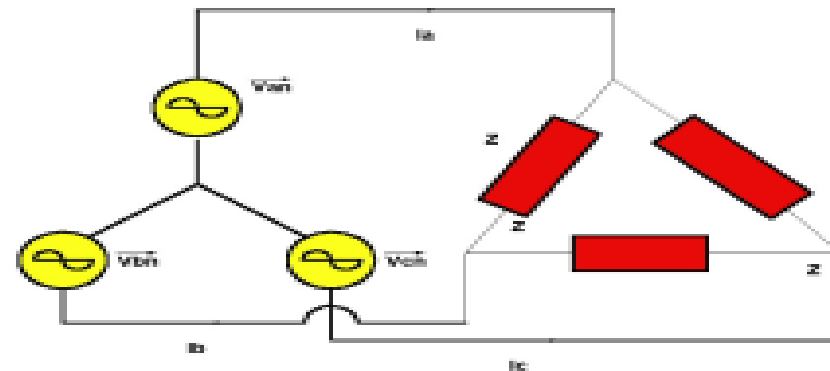

Balanced Δ Loads

Delta-Connected System

The line currents are:


$$\mathbf{I}_a = \mathbf{I}_{ab} - \mathbf{I}_{ca}$$


$$\mathbf{I}_b = \mathbf{I}_{bc} - \mathbf{I}_{ab}$$

$$\mathbf{I}_c = \mathbf{I}_{ca} - \mathbf{I}_{bc}$$

- In a balanced case the line currents are:
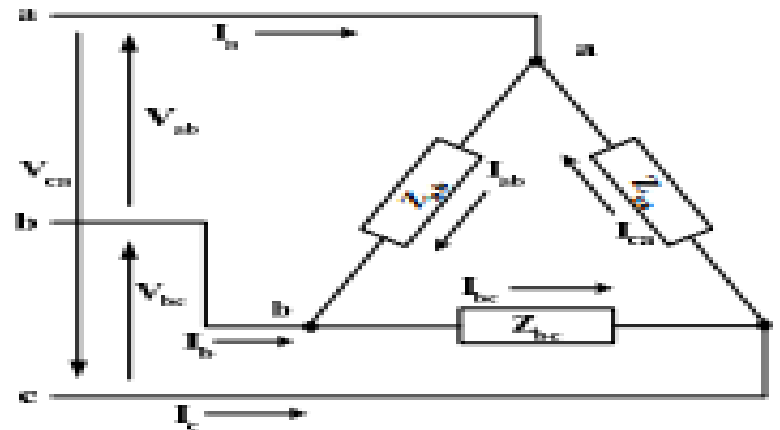
$$I_{line} = \sqrt{3}I_{phase} \angle -30^\circ$$



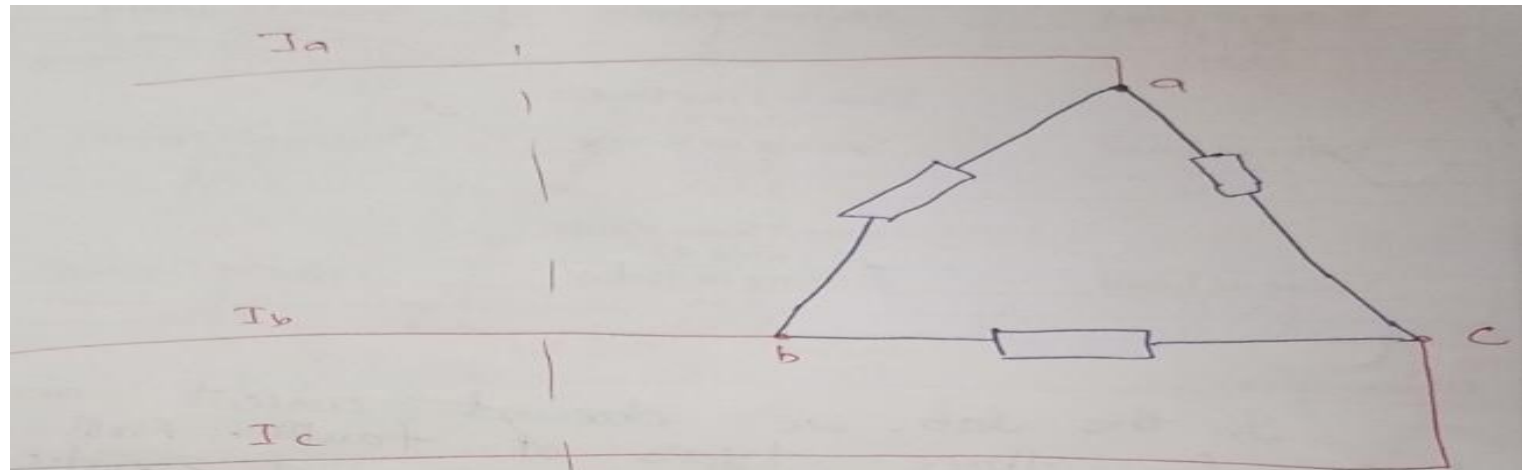

← Line →

$$I_a = I_{ab} - I_{ca}$$

$$I_b = I_{bc} - I_{ab}$$


$$I_c = I_{ca} - I_{bc}$$

$$I_{\text{line}} = \sqrt{3} I_p \angle -30^\circ$$

Balanced Δ Loads

Delta-Connected System

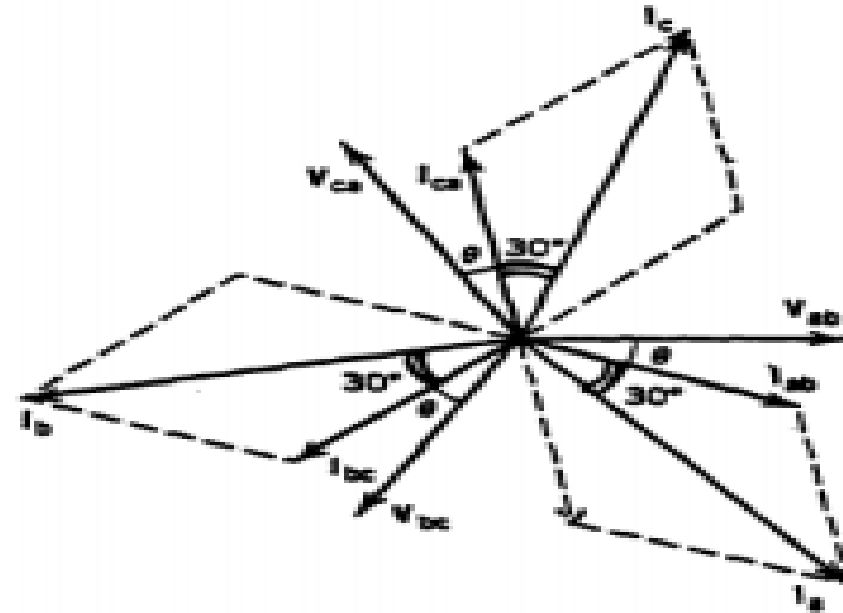- The phasor diagram is used to visualize the system currents
- The system has two type of currents: line and phase currents.
- The delta system has only line-to-line voltages, that are shifted by 30
- The phase currents lead the line currents by 30
- The line current is $\sqrt{3}$ times the phase current and shifted by 30 degree.



Three-phase Circuit

Power Calculation

- The three phase power is equal the sum of the phase powers

$$P = P_a + P_b + P_c$$

- If the load is balanced:

$$P = 3 P_{\text{phase}} = 3 V_{\text{phase}} I_{\text{phase}} \cos(\phi)$$

- Wye system: $V_{\text{phase}} = V_{\text{LN}}$ $I_{\text{phase}} = I_L$ $V_{\text{LL}} = \sqrt{3} V_{\text{LN}}$

$$P = 3 V_{\text{phase}} I_{\text{phase}} \cos(\phi) = \sqrt{3} V_{\text{LL}} I_L \cos(\phi)$$


- Delta system: $I_{\text{Line}} = \sqrt{3} I_{\text{phase}}$ $V_{\text{LL}} = V_{\text{phase}}$


$$P = 3 V_{\text{phase}} I_{\text{phase}} \cos(\phi) = \sqrt{3} V_{\text{LL}} I_L \cos(\phi)$$

Balanced Δ –Y Loads

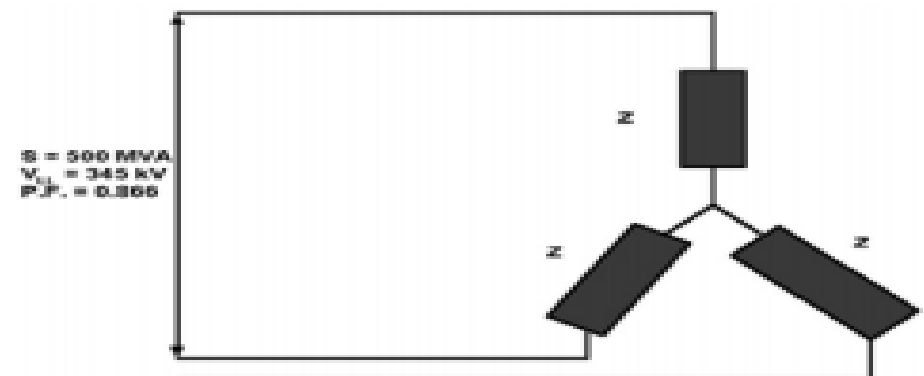Example 1: A 345 kV, three phase transmission line delivers 500 MVA, 0.866 power factor lagging, to a three phase load connected to its receiving end terminals. Assume the load is Y connected and the voltage at the receiving end is 345 kV, find:

- ☐ The load impedance per phase.
- ☐ The line and phase currents.
- ☐ The total real and reactive power.




$$(a) \ Z_{\phi} = \frac{V_{\phi}}{I_{\phi}}$$

$$V_{\phi} = \frac{345 \text{ kV}}{\sqrt{3}} \angle 0^{\circ}, |I_{\phi}| = \frac{S}{\sqrt{3}V_L} = \frac{500 \text{ MVA}}{\sqrt{3} 345 \text{ kV}} = 836.7 \text{ A}$$

$$I_{\phi} = 836.7 \angle -\cos^{-1}(0.866) = 836.7 \angle -30^{\circ}$$


$$Z_{\phi} = 238 \angle 30^{\circ} = 206 + j119$$

$$(b) \ I_L = I_{\phi} = 836.7 \angle -30^{\circ}$$

$$(c) \ P = \sqrt{3}V_L I_L \cos(\theta) = 433 \text{ MW}$$

$$Q = \sqrt{3}V_L I_L \sin(\theta) = 249.9 \text{ MVAR}$$
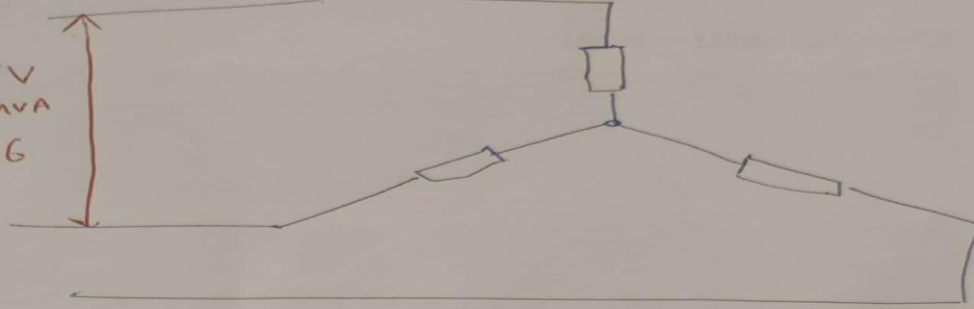
$$\begin{aligned} V_L &= 345 \text{ KV} \\ S &= 500 \text{ MVA} \\ Q &= 866 \end{aligned}$$



(a)

$$Z_{\phi} = \frac{V_{\phi}}{I_{\phi}}$$

$$V_{\phi} = \frac{345 \text{ KV}}{\sqrt{3}}$$

$$I_{\phi} = ?$$

$$S = 3 I_{\phi} V_{\phi}$$

$$S = \sqrt{3} V_L I_L$$

$$I_L = \frac{S}{\sqrt{3} V_L}$$

$$I_L = I_{\phi}$$

$$I_{\phi} = \frac{S}{\sqrt{3} V_L}$$

$$I_{\phi} = 836.7 \angle -30$$

$$Z_{\phi} = \frac{V_{\phi}}{I_{\phi}} = 238 \angle 30^{\circ}$$

(b)

$$I_L = I_{\phi} = 836.7 \angle -30^{\circ}$$

(c)


$$P = \sqrt{3} V_L I_L \cos \theta = 433 \text{ MW}$$

$$Q = \sqrt{3} V_L I_L \sin \theta = 249.9 \text{ MVAR}$$

Balanced Δ –Y Loads

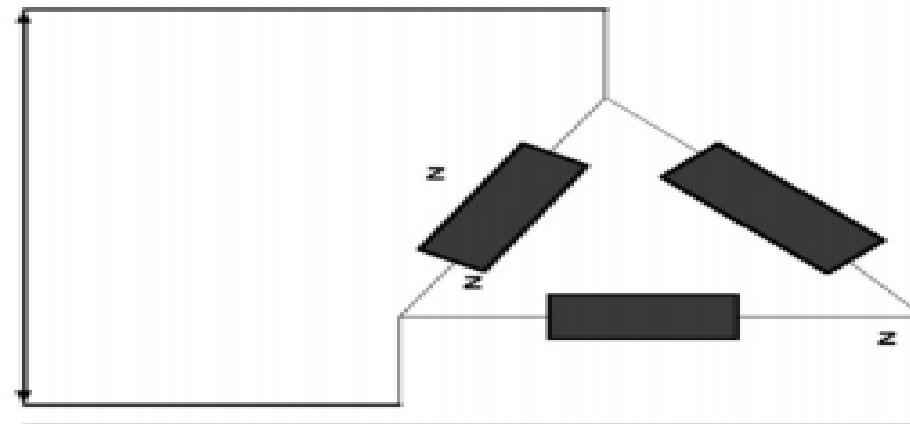Example 2: Repeat example 1 assuming the load is Delta connected.

$S = 500 \text{ MVA}$
 $V_{LL} = 345 \text{ kV}$
 $P.F. = 0.866$



$$(a) \ V_{\phi} = V_L = 345 \text{ kV} \angle 0^\circ,$$

$$|I_{\phi}| = \frac{S}{3V_L} = \frac{500 \text{ MVA}}{3 * 345 \text{ kV}} = 483.1 \text{ A}$$


$$I_{\phi} = 483.1 \angle -\cos^{-1}(0.866) = 483.1 \angle -30^\circ$$

$$Z_{\phi} = \frac{V_{\phi}}{I_{\phi}} = 714 \angle 30^\circ = 618.3 + j357$$

$$(b) \ I_L = \sqrt{3} I_{\phi} \angle -30^\circ = 836.7 \angle -60^\circ$$

$$(c) \ P = \sqrt{3} V_L I_L \cos(\theta) = 433 \text{ MW}$$

$$Q = \sqrt{3} V_L I_L \sin(\theta) = 249.9 \text{ MVAR}$$



Advantages of Balanced Three Phase Versus Single Phase System

- ❑ Smooth flow of power (instantaneous power is constant).
- ❑ Constant torque (reduced vibrations).
- ❑ The power delivery capacity tripled (increased by 200%) by increasing the number of conductors from 2 to 3 (increased by 50%).

